E			Reg. No. :											
	Question Paper Code: 55029													
Ph.D COURSE WORK EXAMINATION, MAY 2018														
	Elective													
Course Work														
15PPE529- APPLICATION OF INTELLIGENT CONTROLLERS FOR POWER OUALITY														
IMPROVEMENT														
(Regulation 2015)														
Duration: Three hours Maximum: 100 Marks												3		
Answer ALL Questions														
PART - A (5 x 20 = 100 Marks)														
1.	(a)	Explain with the help of necessary waveforms the operation of single phase full bridge inverter.							C	CO1-U			20)	
Or														
	(b)	Discuss about various electrical disturbances which affects the power quality.							C	CO1-U			20)	
2.	(a)	Compare the performance of Right and Left shunt control of UPQC with suitable system.							C	CO2- Ana			20)	
$\cap r$														
	(b)	Discuss in detail abo voltage and currents	out the DVR used for	analy	zing	non	sinus	soida	al C	CO2-	Ana	(	20)	
3.	(a)	Explain how the det swell in the power s	w the detection algorithms are used to find the sag and power system.							CO3-U (2			20)	
			Or											
(b) Explain the construction and operating principle of Solid Stat Current Limiter with neat diagram.								te	C	CO3-1	U	(	20)	

4. (a) Design a passive filter to filter out the higher order harmonics in CO4-Ana (10) the electronics system.

Or

(b) Demonstrate the optimal filter design using ANN. CO4-Ana (20)

5. (a) Design a Fuzzy logic controller by using adaptive critic method CO5- Ana (20) for control the STATCOM.

Or

(b) Develop a simulation model for STATCOM operated in voltage CO5- Ana (20) control mode and VAR control mode and discuss the performance of each mode.