

E

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: 52S02

M.E. DEGREE EXAMINATION, MAY 2018

Second Semester

Power Electronics and Drives

15PPE202 - DC Drives and Control

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART - A (5 x 20 = 100 Marks)

1. (a) (i) Draw speed –torque characteristics of DC series motor CO1- U (3)
(ii) What do you understand by Constant torque and Constant power drive? CO1- U (3)
(iii) Explain static Ward Leonard control method in speed control of DC motor CO1- U (14)

Or

- (b) (i) List the types of speed control methods employed in DC motor. CO1- U (4)
(ii) What is meant by Regenerative braking? CO1- U (2)
(iii) Describe multi quadrant operation of DC motor in hoist application. CO1- U (14)

2. (a) (i) List the drawbacks of rectifier fed dc drives. CO2-U (3)
(ii) What is the function of free wheeling diode? CO2- U (3)
(iii) Explain the operation of a single phase fully controlled converter fed separately excited DC motor with neat waveforms and derive the speed torque characteristics. CO2- U (14)

Or

- (b) (i) Write the expression for the average output voltage of a single phase and three phase full converter fed DC drive. CO2- U (2)
(ii) When is discontinuous conduction mode expected with the operation of converter fed DC drives? CO2- U (2)

(iii) With neat diagram explain the various schemes used in multi-quadrant operation of separately excited dc motor with regenerative braking. CO2-U (16)

3. (a) (i) What are the methods of control strategies of chopper control? Which is best suited for DC motor control? CO3-U (4)
- (ii) Explain the operation of the two quadrant chopper fed DC drive system. CO3-U (16)

Or

- (b) (i) What is Time ratio control? CO3-U (2)
- (ii) What are the advantages of operating choppers at high frequency? CO3-U (4)
- (iii) Analyze the principle of operation of class A chopper control separately excited DC motor. CO3-Ana (14)

4. (a) (i) Give the transfer function of converter. CO4-U (2)
- (ii) Mention the types of current controllers. CO4-U (2)
- (iii) Derive the transfer function of DC motor- load and converter system. CO4-App (16)

Or

- (b) (i) Give the transfer function relating speed and field current of a DC motor. CO4-U (4)
- (ii) Derive the transfer function of the speed controller. CO4-App (16)

5. (a) (i) Write any two applications of microcomputer based motor drives. CO5-U (2)
- (ii) Define phase Locked Loop control of dc drives. CO5-U (2)
- (iii) Describe the dc motor speed control using phase locked loop technique. CO5-U (16)

Or

- (b) (i) Write the methods of speed detection. CO5-U (2)
- (ii) What do you mean by digital control of dc drive? CO5-U (2)
- (iii) With block diagram, explain micro-computer control of DC drives. CO5-U (16)