

E

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: 52003

M.E. DEGREE EXAMINATION, MAY 2018

Second Semester

Power Electronics and Drives

15PPE203 – AC DRIVES AND CONTROL

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART - A (5 x 20 = 100 Marks)

1. (a) (i) Explain the principle of v/f control in induction motor drives. CO1- U (8)
(ii) Draw the slip –Torque characteristics of 3 phase Induction Motor. CO1- U (8)
(iii) State the various speed control methods of induction motor. CO1- U (4)
- Or
- (b) (i) Explain about stator voltage control of induction motor drive System. CO1- U (10)
(ii) Explain about torque production in Induction motor. CO1- U (10)
2. (a) (i) Explain the operation of six pulse VSI and CSI fed IM drive. CO2- U (10)
(ii) Draw the control and power schematics of the volts/Hz drive that uses a PWM Inverter. CO2- U (10)
- Or
- (b) (i) Explain in detail about four quadrant control and closed loop operation of AC voltage Controllers. CO2- U (15)
(ii) State the disadvantages of ac voltage controllers. CO1- U (5)
3. (a) (i) Draw the schematic of static scherbius drive and explain its operation. CO3- U (12)
(ii) Explain about power factor considerations modified Kramer drives. CO3- U (8)

Or

- | | | | |
|-----|---|----------|------|
| (b) | (i) Explain about power factor consideration in static scherbius drive system. | CO3- U | (12) |
| | (ii) Analyze equivalent circuit of static static scherbius drive system. | CO3- Ana | (8) |
| 4. | (a) | | |
| | (i) Write briefly about Flux vector estimation method. | CO4- U | (12) |
| | (ii) Explain about indirect feed forward vector control. | CO4- U | (8) |
| | Or | | |
| | (b) | | |
| | (i) Explain about DC drive analogy. | CO4- U | (10) |
| | (ii) Explain the control strategy of DTC. | CO4- U | (10) |
| 5. | (a) | | |
| | Develop the equivalent circuit of a wound field cylindrical rotor synchronous motor also derive the performance equations of the drive. | CO5-App | (20) |
| | Or | | |
| | (b) | | |
| | (i) Explain about control of load commutated synchronous motor drive. | CO5-U | (12) |
| | (ii) Explain about speed control of synchronous motor drive. | CO5-U | (8) |
-