

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 41433

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2017

Third Semester

Electronics and Communication Engineering

14UEC303 - CIRCUIT THEORY

(Regulation 2014)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- The number of independent loops for a network with n nodes and b branches is
 - $n-1$
 - $b-n$
 - $b-n+1$
 - independent for the number of nodes
- Ohm's law is given by
 - $V = ZI$
 - $I = GV$
 - both (a) and (b)
 - none of these
- Superposition theorem is not applicable to networks containing
 - nonlinear elements
 - dependent voltage source
 - dependent current source
 - transformers
- Maximum power gets transferred to the load when the load impedance is
 - equal to zero
 - equal to one
 - equal to source impedance
 - none of the above
- What is the Q (Quality factor) of a series circuit that resonates at 6 kHz , has equal reactance of 4 kilo-ohms each, and a resistor value of 50 ohms ?
 - 0.001
 - 50
 - 80
 - 4.0
- The Q -factor in a series R-LC circuit at resonance is
 - $\frac{1}{R} \sqrt{\frac{C}{L}}$
 - $\frac{1}{L} \sqrt{\frac{C}{R}}$
 - $\frac{1}{R} \sqrt{\frac{L}{C}}$
 - $\frac{1}{R^2} \sqrt{\frac{C}{L}}$


7. Self-inductance of a magnetic coil is proportional to
 (a) N (b) $1/N$ (c) N^2 (d) $1/N^2$
8. In two wattmeter method of power measurement, when the power factor of load is zero leading or lagging the two wattmeter will give _____ reading.
 (a) Zero (b) equal
 (c) equal and opposite (d) not equal
9. A two - port network is symmetrical if
 (a) $Z_{11}Z_{22} - Z_{12}Z_{21} = 1$ (b) $AD - BC = 1$
 (c) $h_{11}h_{22} - h_{12}Z_{21} = 1$ (d) $Y_{11}Y_{22} - Y_{12}Y_{21} = 1$
10. For a two port network to be reciprocal
 (a) $Z_{11}=Z_{22}$ (b) $y_{21}=y_{22}$ (c) $h_{21}= - h_{12}$ (d) $AD-BC=0$

PART - B (5 x 2 = 10 Marks)

11. State Kirchhoff's laws for electric circuits.
12. Write the expression for Millman's equivalent source of n number of parallel connected voltage sources.
13. Give the expressions for series and parallel resonance frequency.
14. Write the symmetrical components of three phase system.
15. Write the expression of Y parameters in terms of ABCD parameters.

PART - C (5 x 16 = 80 Marks)

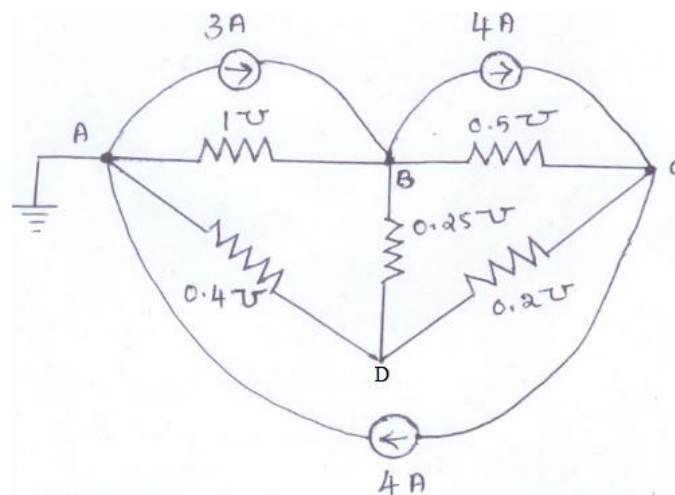16. (a) Find V_{BD} by nodal analysis for the circuit shown in the figure. (16)



Or

- (b) Find the equivalent resistance between the terminals A and B for the circuit shown in Figure 3. (16)

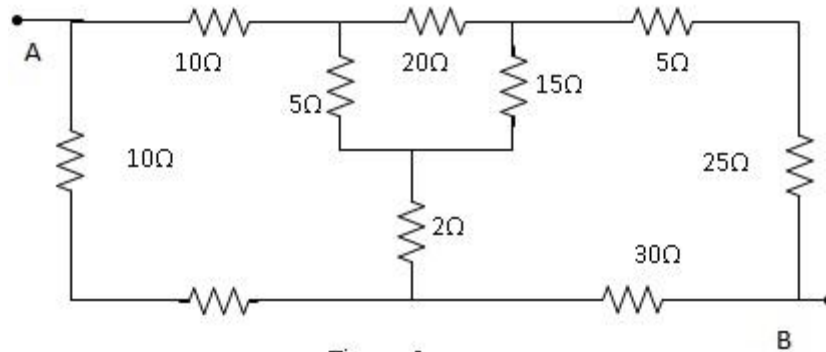


Figure 3

17. (a) Determine the current in the 10-Ω resistor for the circuit shown in Figure 4 by using superposition theorem. (16)


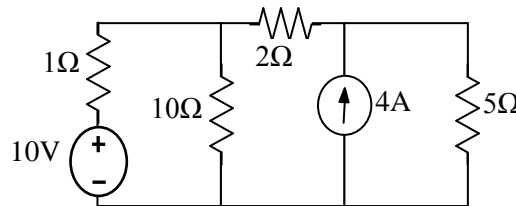


Figure 4

Or

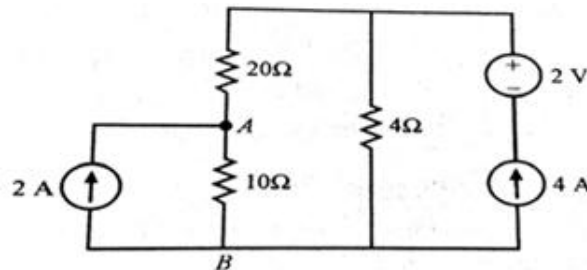- (b) Determine V_{AB} using superposition theorem in the circuit shown in figure. (16)



18. (a) A RLC series circuit consists of $R = 16 \Omega$, $L = 5 \text{ mH}$ and $C = 2 \mu\text{F}$. Calculate the quality factor, bandwidth and half-power frequencies. (16)

Or

- (b) Obtain the resonant frequency, Q-factor, band width and the voltage across the capacitor at resonance for the series RLC circuit having $R = 7.5\Omega$, $L = 6\mu H$ and $C = 40pF$, with a supply voltage of 0.5 volts. (16)
19. (a) Two coils connected in series have an equivalent inductance of 0.8 H when connected in aiding and an equivalent inductance of 0.4 H when connected in opposing. Determine the mutual inductance. Calculate the self-inductance of the coils, by taking $k = 0.55$. (16)

Or

- (b) Three pure resistances value 200 Ω each are connected to a 3 phase, 440 V, 50 Hz supply. Determine the line, phase values of current, voltage and active power in both star and delta connections. (16)
20. (a) The current I_1 and I_2 at the input port and output port respectively of a two port network are given by
- $$I_1 = 6V_1 - V_2 \text{ and } I_2 = -V_1 + 2V_2$$
- Find the equivalent pie-network and the input impedance when a load of $(4+j7)\Omega$ is connected across the output port. (16)

Or

- (b) Design a low pass filter having cut – off frequency of 2 KHz, to operate with a terminal load resistance of 500 Ω . (16)
-