

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: 52521

M.E. DEGREE EXAMINATION, MAY 2017

Second Semester

Power Electronics and Drives

15PPE201 - ANALYSIS OF INVERTERS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 20 = 100 Marks)

1. (a) (i) Explain with the help of waveforms the operation of a single phase half bridge inverter. (12)
 - (ii) List techniques employed for the reduction of harmonics from the output voltage of an inverter. (4)
 - (iii) Explain the need of connecting diodes in anti-parallel with switches. (4)
- Or
- (b) (i) Describe modified McMurray half bridge inverters with appropriate voltage and current waveforms. Derive the expressions for the commutating components L and C. (12)
 - (ii) What are the advantages and disadvantages of PWM? (4)
 - (iii) Draw circuit of auxiliary-commutated single phase bridge inverter. (4)
2. (a) (i) With necessary diagram describe the space vector modulation used to control the output voltage of three phase inverter. (12)
 - (ii) Draw the sinusoidal pulse-width modulation of three phase inverter. (4)
 - (iii) Explain limiting factor for the operating frequency of an inverter. (4)

Or

- (b) (i) With necessary diagram describe the sinusoidal, multi pulse used to control the output voltage of three phase inverter (12)
- (ii) Draw the basic diagram of three phase bridge inverter. (4)
- (iii) Define harmonic conduction by single-pulse width modulation. (4)
3. (a) (i) Describe elaborately the single phase auto sequential commutated CSI with relevant mode d diagrams and waveforms. (12)
- (ii) What is partial and full overlapping in a three phase auto sequential commutated inverter. (4)
- (iii) Compare VSI and CSI. (4)

Or

- (b) (i) Describe in detail the operation of load commutated inverter. (12)
- (ii) What are the applications of CSI? (4)
- (iii) What is the purpose of hysteresis modulation. (4)
4. (a) (i) With neat diagram describe the operation of cascaded multilevel inverter. (12)
- (ii) What are the features of cascaded inverter? (4)
- (iii) List the applications of multilevel inverter. (4)

Or

- (b) (i) Drive and explain the flying capacitor multilevel inverter. (12)
- (ii) What does the capacitor voltage UN balancing means? (4)
- (iii) What are the advantages and disadvantages of flying capacitor? (4)
5. (a) (i) Drive and explain the series resonant inverters with unidirectional switches. (12)
- (ii) List the advantages of parallel resonant inverters. (4)
- (iii) Define Class E resonant inverter. (4)

Or

- (b) (i) Drive and explain the frequency response of series resonant inverters . (12)
- (ii) Explain the principal of zero-voltage switching resonant converters. (8)