

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 50329**

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2017

Second Semester

Electrical and Electronics Engineering

15UEE209 - ELECTRIC CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Kirchhoff's law is applicable to
  - AC circuits only
  - DC circuits only
  - AC as well as DC circuits
  - Passive networks only
- Two resistances are connected in parallel and each dissipates 40 watts. The total power supplied by the source equals
  - 40 watts
  - 80 watts
  - 160 watts
  - 20 watts
- The super position theorem applicable to
  - current only
  - voltage only
  - both current and voltage
  - current, voltage and power
- A star circuit has each element of resistance  $\frac{R}{2}$ . The equivalent delta elements will be
  - R
  - 3R
  - $\frac{3}{2}R$
  - $\frac{R}{6}$
- In a parallel resonant circuit, the impedance is
  - maximum
  - minimum
  - equal to difference of inductive and capacitive impedances
  - none of these


6. A coil with 1000 turns carrying a current of 8 amps produces a flux of  $6 \times 10^{-8}$  weber. The inductance of the coil will be
- (a) 0.00075 H      (b) 0.0075 H      (c) 0.075 H      (d) 0.75 H
7. A DC voltage  $V$  is applied to series RL circuit at time  $t = 0$ . The current at time  $t$  is
- (a)  $\frac{V}{R} \varepsilon^{-Rt/L}$       (b)  $\frac{V}{R} (1 - \varepsilon^{-Rt/L})$
- (c)  $\frac{V}{R} \varepsilon^{Rt/L}$       (d)  $\frac{V}{R} (1 - \varepsilon^{Rt/L})$
8. A DC voltage  $V$  is applied to series RC circuit at time  $t = 0$ . The current at time  $t$  is equal to
- (a)  $\frac{V}{R} \varepsilon^{-t/RC}$       (b)  $\frac{V}{R} \varepsilon^{t/RC}$
- (c)  $\frac{V}{R} (1 - \varepsilon^{-t/RC})$       (d)  $\frac{V}{R} (1 - \varepsilon^{t/RC})$
9. The minimum number of wattmeter required to measure power in a 3 phase unbalanced star connected load is
- (a) four      (b) three      (c) two      (d) one
10. If the power factor of the three phase load is 0.5, then one of the wattmeter will read
- (a)  $\frac{\sqrt{3}W}{2}$       (b)  $\frac{W}{\sqrt{3}}$       (c)  $\frac{W}{2}$       (d) zero

PART - B (5 x 2 = 10 Marks)

11. State ohms law.
12. Define dual networks.
13. What is meant by tuned circuit?
14. What is transient?
15. Give the line and phase values in star connection.


PART - C (5 x 16 = 80 Marks)

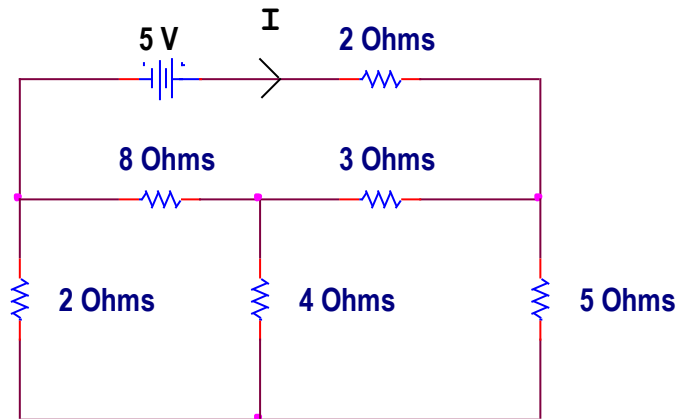16. (a) Find the current  $I$  in the network shown below. (16)




Or

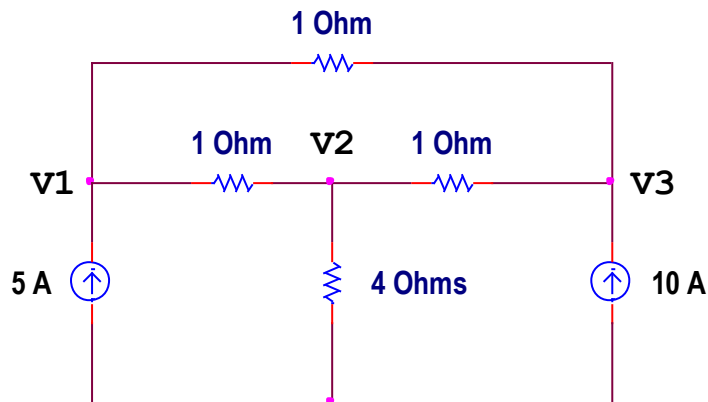- (b) Find the node voltages  $V_1$ ,  $V_2$ ,  $V_3$  by the nodal method for the circuit given below. (16)




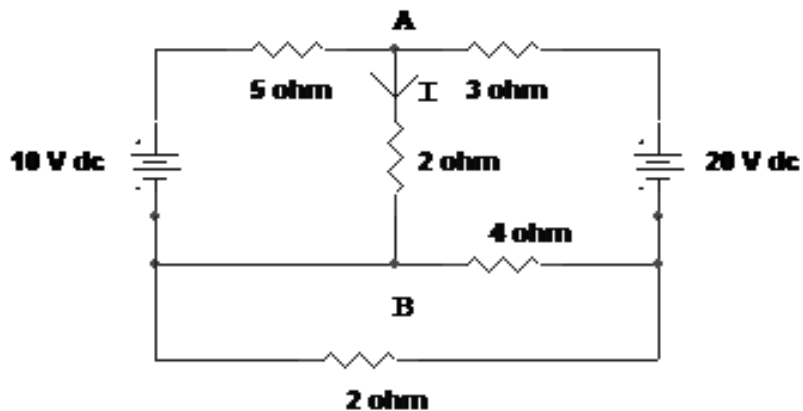17. (a) Find the current in the 2 ohm resistor between A and B for the network using superposition theorem. (16)



Or

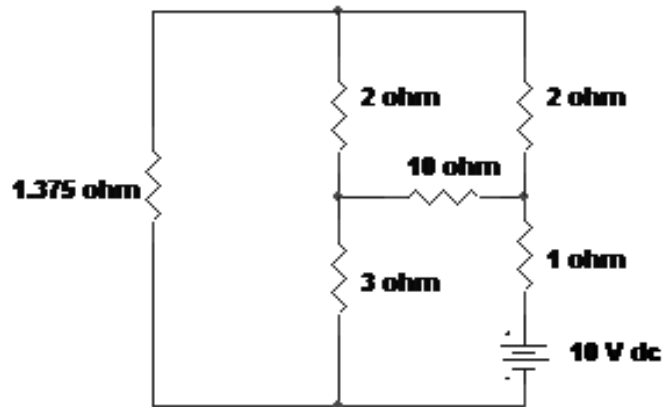- (b) For the circuit shown in the diagram below, find  $I_3$  and verify reciprocity theorem. (16)



18. (a) Obtain the expression for self inductance, mutual inductance and coefficient of coupling in magnetic circuit. (16)

Or

- (b) Perform the analysis of single tuned coupled circuits. (16)
19. (a) Perform the analysis of RL transient circuit for both rise of current and decaying transient. (16)

Or

- (b) A series RLC circuit with  $R = 300 \text{ Ohms}$ ,  $L = 1 \text{ Henry}$  and  $C = 100 \times 10^{-6} \text{ Farad}$  has a constant voltage of  $50 \text{ V}$  applied to it at  $t = 0$ . Find the value of current. (16)
20. (a) Explain the two wattmeter method of measurement of three phase power with phasor diagram. (16)

Or

- (b) Explain the line and phase values of three phase system in both star and delta connection. (16)