

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 21008

B.E. / B.Tech. DEGREE EXAMINATION, OCTOBER 2014.

Second Semester

Computer Science and Engineering

01UCS207- DIGITAL PRINCIPLES AND SYSTEM DESIGN

(Common to Information Technology)

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions.

PART A - (10 x 2 = 20 Marks)

1. Realize OR gate using only NAND gates.
2. Subtract $(1010)_2$ from $(1000)_2$ using 2's complement method.
3. Convert the given number $(0110)_2$ into i) Gray code and ii) Excess-3 code.
4. Write a gate level HDL description for the full adder circuit.
5. Compare a Decoder with a De-multiplexer.
6. Determine the number of address lines required for accessing 2MB and a 64KB memory.
7. Show how a JK flip flop can be operated as a toggle flip flop.
8. State the differences between combinational logic and sequential logic.
9. What is a critical race? State its importance in an asynchronous sequential circuit.
10. List the assumptions that must be made for a fundamental mode circuit.

PART - B (5 x 16 = 80 Marks)

11. (a) (i) Simplify the following Boolean expression.

$$Y = \overline{\overline{A\overline{B}} + ABC} + A(B + \overline{A\overline{B}}) \quad (8)$$

(ii) Simplify the following boolean function using K-map method.


$$F(A,B,C,D,E) = \sum m(1,5,7,13,14,15,17,18,21,22,25,29) + \sum d(6,9,19,23,30) \quad (8)$$

Or

(b) Find the minimal sum of products for the Boolean expression,

$$F(w,x,y,z) = \sum m(1,3,4,5,9,10,11) + \sum d(6,8) \text{ using Quine - Mc Cluskey tabulation method.} \quad (16)$$

 12. (a) Analyze the combinational circuit shown in Fig. 12(a) to determine the boolean expressions and the truth table governing the outputs of the circuit.



(16)

Or

(b) (i) Design a combinational logic circuit to compare two 2-bit binary numbers A and B and to check whether $A < B$, $A = B$ or $A > B$. (8)

(ii) Explain the BCD adder with a neat block diagram. (8)

13. (a) (i) Implement the function, $F(A,B,C,D) = \sum m(0,1,2,5,6,9,12,14)$ using two 4x1 multiplexers. (8)

(ii) Write a structural Verilog description for a 2x4 decoder with a neat sketch. (8)

Or

(b) A combinational logic circuit is defined by the following functions:

$$F_1(x,y,z) = \sum m(1,2,4,6)$$

$$F_2(x,y,z) = \sum m(0,1,6,7)$$

$$F_3(x,y,z) = \sum m(2,6)$$

$$F_4(x,y,z) = \sum m(1,2,3,5,7)$$

Implement the circuit using a PLA with 3 inputs, 7 product terms and 4 outputs. (16)

14. (a) With suitable examples explain state reduction and state assignment of sequential circuits. (16)

Or

(b) (i) Design a 3 bit binary Up Counter using JK flip flops. (10)

(ii) Write the HDL description of a T flip flop and a JK flip flop from D flip flop. (6)

15. (a) (i) Discuss the need and operation of a De-bounce circuit with a neat diagram. (6)

- (ii) Determine whether the circuit in Fig. 15(a) has a static hazard or not. If yes, design a hazard free logic for the same input and output relation.

 


Fig. 15(a)

(16)

Or

- (b) (i) Briefly describe about race free assignment in asynchronous sequential circuits. (8)
- (ii) Write short notes on hazards in combinational and sequential circuits. (8)