

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: U2E05**

B.E./B.Tech. DEGREE EXAMINATION, MAY 2024

Second Semester

Artificial Intelligence & Data Science

21UAD205- Digital Logic Design

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

1. Conversion of decimal number 5610 to its binary number equivalent is CO1- R  
(a) 1100112      (b) 110011102      (c) 1110002      (d) 111112
2. How many full adders required to design a 4-bit binary parallel adder CO2- R  
(a) 1      (b) 2      (c) 3      (d) 4
3. Which of the following flip-flops is free from the race-around problem? CO1- R  
(a) T flip-flop      (b) SR flip-flop      (c) Master-Slave Flip-flop      (d) flip-flop
4. In a synchronous circuit, the present state is determined by CO1- R  
(a) unclocked flip-flops      (b) clocked flip-flops      (c) flip-flops      (d) latches
5. For programmable logic functions, which type of PLD should be used? CO1- U  
(a) PLA      (b) PAL      (c) CPLD      (d) SLD

PART – B (5 x 3 = 15 Marks)

6. Subtract the following 11011-11001 using 2's complement CO3- App
7. Write the Gray code and excess -3 code for the binary code 1010 CO3- App
8. Define Priority encoder with truth table and circuit CO1- R
9. List the basic types of shift registers in terms of data movement. CO1- R

10. Given  $F(A, B, C) = \sum m(1, 5, 6, 7)$ . CO3- App

Realize the hazard free circuit for the above function.

PART – C (5 x 16= 80 Marks)

11. (a) Design K map and minimize using K map method. Implement it using NAND gates CO3-App (16)

$$F(A,B,C,D) = \pi (0,1,4,5,6,8,9,12,13,14)$$

Or

(b) Reduce the following equation using Quine McClucky method of minimization CO3-App (16)

$$F(A,B,C,D) = m(0,1,3,4,5,7,10,13,14,15)$$

12. (a) Design a circuit for parallel addition and subtraction CO3-App (16)

Or

(b) Design a circuit for priority encoder CO3-App (16)

13. (a) Using SR flip flops, design a parallel counter which counts in sequence CO3-App (16)

$$000,111,101,110,001,010,000 \dots\dots\dots$$

Or

(b) Design MOD-10 Synchronous counter using JK flip-flops.  $\forall$  execution table and State table CO3-App (16)

14. (a) Give hazard– free realization for the following Boolean function CO3-App (16)

$$f(A,B,C,D) = \pi (0,2,6,7,8,10,12)$$

Or

(b) Give hazard– free realization for the following Boolean function CO3-App (16)

$$f(A,B,C,D) = \pi (3,4,7,8,9,12,15)$$

15. (a) Explain in detail about the classification of memories with neat diagram? CO3-App (16)

Or

(b) Implement the following functions using PLA. CO3-App (16)

$$F1(A, B, C) = \sum m(1, 2, 4, 6)$$

$$F2(A, B, C) = \sum m(0, 1, 6, 7)$$

$$F3(A, B, C) = \sum m(2, 6)$$