

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: R2E05**

B.E./B.Tech. DEGREE EXAMINATION, MAY 2024

Second Semester

Artificial Intelligence and Data Science

R21UAD205- DIGITAL LOGIC DESIGN

(Common to CSE(AI&ML) Engineering branches)

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (10 x 2 = 20 Marks)

1. To Perform Excess-3 Addition for the given number: 16 and 29 CO2-App
2. What is meant by weighted and non-weighted coding? CO1-U
3. Write down the applications of Multiplexer CO1-U
4. Draw the circuit of half-adder. CO1-U
5. Define Shift Register CO1-U
6. Write short note on Bistable Multivibrator CO1-U
7. What do you mean by Race condition? CO1-U
8. What are the different types of shift type? CO1-U
9. Differentiate ROM and RAM CO1-U
10. Define EEPROM CO1-U

PART – B (5 x 16= 80 Marks)

11. (a) Reduce the following 4 variable function to its minimum sum of products form: CO2-App (16)

Y

$$= \bar{A}\bar{B}\bar{C}\bar{D} + ABC\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D + AB\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D$$

Or

- (b) 1.Hexadecimal to Octal Conversion – 4marks CO2-App (16)  
     i) (BC66.AF)<sub>16</sub>  
     ii) (9C)<sub>16</sub>  
 2. Decimal to Octal– 4 marks  
     i) (12.125)<sub>10</sub>  
     ii) (62.025)  
 3.Hexadecimal to binary – 4 marks  
     i. (70)<sub>16</sub>  
     ii. (B2F)<sub>16</sub>  
 4.Octal to Decimal- 4 marks  
     i) (7423)<sub>8</sub>  
     ii) (2345.23)<sub>8</sub>
12. (a) Implement the following Boolean function using 8:1 multiplexer CO2-App (16)  

$$F(A,B,C,D)=\overline{A}B\overline{D}+ACD+\overline{B}CD+\overline{A}C\overline{D}$$
     Or  
 (b) Implement the following Boolean function using 8:1 multiplexer CO2-App (16)  

$$F(A,B,C,D)=\sum m(0,2,3,4,6,9,11,14,15)$$
13. (a) Explain the steps in designing synchronous sequential circuits. CO1-U (16)  
     Or  
 (b) Discuss about Master Slave flip flop and Set Reset flip flop CO1-U (16)
14. (a) Briefly Explain about Threats and types CO1-U (16)  
     Or  
 (b) Discuss about State Reduction and flow table. CO1-U (16)
15. (a) Explain in detail about the classification of memories with neat diagram? CO1-U (16)  
     Or  
 (b) Explain in Detail about Error-Free data CO1-U (16)