

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: U3B06

B.E./B.Tech. DEGREE EXAMINATION, APRIL 2024

Third Semester

Biomedical Engineering

21UBM306 - DIGITAL LOGIC CIRCUITS

(Regulations 2021)


Duration: Three hours

Maximum: 100 Marks


Answer All Questions

PART A - (10x 2 = 20 Marks)

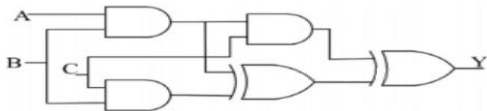1. Express the function $Y = A + B'C$ in canonical POS CO1-App
2. Simplify $(A' + B)(A + B)$ CO1-App
3. The output of the combinational circuit given below is CO1-App



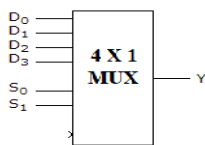4. For the device shown here, let all D inputs be LOW, both S inputs be HIGH, what is the status of the Y output? Explain your answer with an example CO1-App



5. Tabulate the differences between edge triggering and level triggering in sequential circuits. CO2-U
6. Mention the steps for the design of asynchronous sequential circuit CO2-U
7. Define dynamic hazard. When do they occur? CO3-U
8. How to differentiate fundamental mode from pulsed mode asynchronous sequential circuit. CO3-U
9. Why RAMs are called as Volatile? CO4-U
10. Differentiate static and dynamic RAM. CO4-U

PART – B (5 x 16= 80 Marks)

11. (a) Obtain (a) minimal sum of product and (b) minimal product of sum expression for the given below $y = M(1,2,3,7,8,9,10,11,14,15)$ using Karnaugh map method and draw the logic diagram
CO1-App (16)
- Or
- (b) Find a minimal sum-of-products for the Boolean expression $f(w, x, y, z) = \sum m(1,2,3,7,8,9,10,11,14,15)$ using the Quine-McCluskey method.
CO1-App (16)
12. (a) Implement the following Boolean function using an 8:1 multiplexer considering D as the input and A,B,C as selection lines $F(A, B, C, D) = AB' + BD + B'CD'$
CO2-App (16)
- Or
- (b) Write a brief note on the following combinational circuits:
CO2-App (16)
(i) Full adder (ii) Full subtractor
13. (a) Outline the working principle of JK FF and explain the Master/Slave JK FF.
CO3-App (16)
- Or
- (b) Using SR flip flops, design a parallel counter which counts in the sequence 000,111,101,110,001,010,000,...
CO3-App (16)
14. (a) Design an asynchronous sequential circuit with two input X and Y and one output Z. The output $Z=1$ if X1 changes from 0 to 1. $Z=0$ if X2 changes from 0 to 1, and $Z=0$ otherwise.
CO3-App (16)
- Or
- (b) Design a circuit that has no static hazards and implement the Boolean function $F(A,B,C,D) = \sum (0,2,6,7,8,10,12)$ using AND-OR logic.
CO3-App (16)
15. (a) Implementation the following Boolean function using PAL
CO4-Ana (16)
 $W(A,B,C,D) = \sum m(2, 12,13)$
 $X(A,B,C,D) = \sum m(7,8,9,10,11,12,13,14,15)$
 $Y(A,B,C,D) = \sum m(0,2,3,4,5,6,7,8,10,11,15)$
 $Z(A,B,C,D) = \sum m(1,2,8,12,13)$
- Or
- (b) A Combinational Circuit is defined by the function:
CO4-Ana (16)
 $F1 = \sum m(3,5,7)$ $F2 = \sum m(4, 5, 7)$ Implement the circuit with a PLA having 3 inputs, 3 product terms and two outputs

