

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: R2205

B.E./B.Tech. DEGREE EXAMINATION, MAY 2024

Second Semester

Computer Science and Engineering

R21UCS205- DIGITAL ELECTRONICS

(Common to Cyber Security Engineering branch)

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

- Binary addition $0+1$ is equal to _____ CO1- U
(a) 1 (b) 0 (c) 2 (d) 3
- The Full adder is a _____ input and _____ output combinational Circuit CO1- U
(a) 2 and 1 (b) 2 and 2 (c) 3 and 3 (d) 3 and 2
- When both inputs of a J-K flip-flop cycle, the output will _____ CO1- U
(a) Be invalid (b) Change (c) Not change (d) Toggle
- The complexity of the asynchronous circuit is involved in timing problems of CO1- U
(a) inputs (b) Latches (c) feedback path (d) clock pulses
- Which type of device FPGA are? CO1- U
(a) SLD (b) SRAM (c) EPROM (d) PLD

PART – B (5 x 3= 15Marks)

- What is Boolean algebra? CO1- U
- Define Half adder and write its Truth table CO1- U
- What is the application table of a D flip-flop? CO1- U
- What is hazard? CO1- U
- Define PROM. CO1- U

PART – C (5 x 16= 80Marks)

11. (a) Solve the following: CO2 -App (16)
(i) $(1001010.1101001)_2$ to base10
(ii) $(12.32)_{10}$ to base2
(iii) $(101FA)_{16}$ to base10
- Or
- (b) Plot the following Boolean function in Karnaugh map and simplify it in CO2 -App (16)
SOP $F(w,x,y,z) = \sum(7,9,10,11,12,13,14,15)$
12. (a) Design Full subtractor and derive expression for difference and borrow. CO2- App (16)
Cin(X,Y) with circuit diagram .
- Or
- (b) Design Full Adder and derive expression for Sum and Carry in Cin(X,y) with circuit diagram. CO2- App (16)
13. (a) Design of 4 bit Ring counter with the help of state diagram, state table, Excitation table and maps. CO2- App (16)
- Or
- (b) Design of Ripple counter with the help of logic diagram and truth table. CO2- App (16)
14. (a) Why Hazards may happens in the asynchronous sequential circuits and discuss how to avoid Hazards ? CO1- U (16)
- Or
- (b) Explain in detail about races with suitable example? CO1- U (16)
15. (a) Explain the Characteristic function of RTL and ECL circuits in Logic families. CO1- U (16)
- Or
- (b) Discuss in detail about Programmable Logic Devices With the help of its block diagram. CO1- U (16)