

**A**

Reg. No. :

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

**Question Paper Code: R2305**

B.E./B.Tech. DEGREE EXAMINATION, APRIL 2024

Second Semester

Electrical and Electronics Engineering

R21UEE205- ELECTRIC CIRCUIT ANALYSIS

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (10 x 1 = 10 Marks)

1. The resistors values in delta network that is equivalent to a star containing three  $120\ \Omega$  resistors is \_\_\_\_\_ CO1-U  
(a)  $360\ \Omega$  each      (b)  $240\ \Omega$  each      (c)  $180\ \Omega$  each      (d)  $120\ \Omega$  each
2. Which among the following is true about ohm's law? CO1- U  
(a)  $I \propto V$       (b)  $I = V/R$       (c)  $V = IR$       (d) All of these
3. The form factor of sinusoidal wave form is \_\_\_\_\_ CO1-U  
(a) 1.414      (b) 1.11      (c) 0      (d) 1.5
4. The power factor of an AC circuit is equal to CO1-U  
(a) Cosine of the phase angle      (b) Sine of the phase angle  
(c) Unity for a resistive circuit      (d) Unity for a reactive circuit
5. When the power transferred to the load is maximum, the efficiency of power transfer is CO1-U  
(a) 25%.      (b) 100%.      (c) 75%.      (d) 50%
6. Superposition theorem can be applied only to circuits having CO1-U  
(a) Resistive elements      (b) Passive elements  
(c) Nonlinear elements      (d) linear bilateral elements
7. In a series resonance circuit, series resonance occurs when? CO1-U  
(a)  $X_L = 1$       (b)  $X_C = 1$       (c)  $X_L = X_C$       (d)  $X_L = - X_C$


8. The power factor is unity for the \_\_\_\_\_ resonant circuit. CO1-U  
 (a) Series (b) parallel (c) both a & b (d) none
9. In an R-C circuit, when the switch is closed, the response CO1-U  
 (a) do not vary with time (b) decays with time  
 (c) rises with time (d) first increases and then decreases
10. If the roots of an equation are complex conjugate, then the response CO1-U  
 will be?  
 (a) over damped (b) critically damped (c) damped (d) under damped

PART – B (5 x 2= 10 Marks)

11. State Kirchoff's current law CO1 U
12. Define RMS value CO1 U
13. State maximum power transfer theorems CO1 U
14. Determine the resonant frequency of the RLC series circuit with  $R=10\Omega$ ,  $L=0.5\text{mH}$  and  $C = 10\mu\text{F}$ . CO1 U
15. What is the time constant of RL circuit with  $R=10\Omega$  and  $L=20\text{mH}$ . CO1 U

PART – C (5 x 16= 80 Marks)

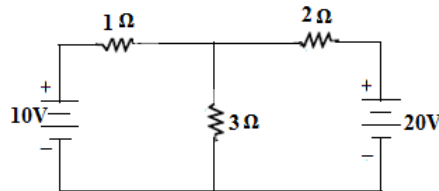
16. (a) Solve the current through  $3\Omega$  resistor in the circuit shown in CO2-App (16)  
 below fig:



Or


- (b) Derive an expression for star connected resistance into delta CO2-App (16)  
 connected resistance.
17. (a) Derive an expression for power and power factor of an RC series CO2- Ana (16)  
 circuit.
- Or
- (b) Two impedance  $Z_1 = (6 + j8)\Omega$  and  $Z_2 = (3 - j4)\Omega$  are CO2- App (16)  
 connected in parallel. This combination is connected across  
 230V, 50HZ AC supply. Calculate the current in each branch,  
 total current and total power consumed by the circuit

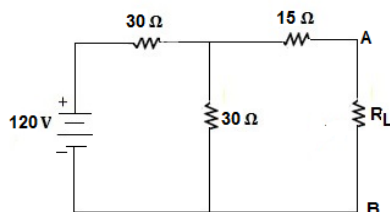18. (a) For the circuit given below calculate the value of the load resistance for maximum power transferred from source to load. Also find the value of maximum power in  $R_L$  CO2- App (16)




Or

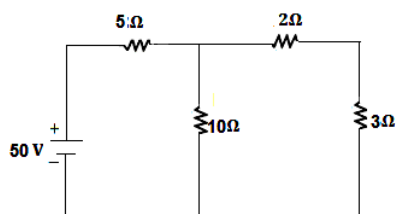- (b) By using Thevenin's theorems to find out current in CO2- App (16)



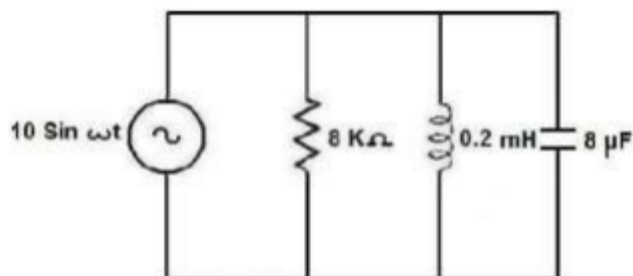19. (a) In the parallel RLC circuit, calculate resonant frequency, bandwidth Q-factor and power dissipated at half power frequencies. CO4-Ana (16)



Or

- (b) Consider an RLC circuit consisting of a resistor (R), inductor (L), and capacitor (C) connected in series. The values of R, L, and C are given as follows:  $R = 5 \Omega$ ,  $L = 40 \text{ mH}$ , and  $C = 1 \mu\text{F}$ . Answer the following questions based on this circuit: CO4-Ana (16)
- Calculate the resonant frequency ( $f_r$ ) of the circuit.
  - Determine the Q-factor (Quality factor) of the circuit.
  - Calculate the bandwidth of the circuit.
  - Half Power frequencies.

20. (a) Consider an RL circuit with a resistor (R) of  $10\ \Omega$  and an inductor (L) of  $0.5\ \text{H}$ . The circuit is initially at rest. At  $t = 0$ , a DC voltage source of  $12\ \text{V}$  is suddenly connected across the circuit. Using Laplace transforms, determine the expression for the current in the circuit and plot its transient response. CO4-Ana (16)

Or

- (b) Consider an RLC circuit consisting of a resistor (R) of  $20\ \Omega$ , an inductor (L) of  $1\ \text{H}$ , and a capacitor (C) of  $10\ \mu\text{F}$ . The circuit is initially at rest. At  $t = 0$ , a sinusoidal voltage source of  $50\ \text{V}$ , with a frequency of  $1\ \text{kHz}$ , is applied across the circuit. Using Laplace transforms, determine the expression for the current in the circuit and plot its transient response. CO4-Ana (16)