

C

Reg. No. :

|  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|

**Question Paper Code: U6402**

B.E. / B.Tech. DEGREE EXAMINATION, APRIL / MAY 2025

Sixth Semester

Electronics and Communication Engineering

21UEC602- VLSI DESIGN

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

1. \_\_\_\_\_ is a language used to describe a digital system CO1-U  
(a) Verilog (b) c program (c) C++ Program (d) Java Program
2. The distance between the source and drain is called CO1-U  
(a) Channel (b) Gate (c) Drain (d) Source
3. The resistance and capacitance product of the MOS transistor is called CO1-U  
(a) intrinsic delay (b) Extrinsic delay (c) both (a) & (b) (d) none of the above
4. Physical and electrical specification is given in \_\_\_\_\_ CO1-U  
(a) architectural design (b) logic design (c) system design (d) functional design
5. High and low noise margins can be equalized by CO1-U  
(a)  $\beta_n = \beta_p$  (b)  $\beta_n$  greater than  $\beta_p$  (c)  $\beta_n$  lesser than  $\beta_p$  (d)  $L_p = 2L_n$

PART – B (5 x 3= 15 Marks)

6. Design a D flip-flop circuit using behavioral level description. CO2 - App
7. Sketch a 3 input NAND gate with transistor widths chosen to achieve effective rise and fall resistance equal to that of a unit inverter(R). CO3 - App
8. Define power dissipation. CO1 – U
9. Design the AND gate using pseudo NMOS logic. CO3- App
10. What is Low Power Logic Styles? CO1 – U


PART – C (5 x 16= 80 Marks)

11. (a) (i) Design 4 bit input device and write a Verilog code for following conditions, it combines 4 bit at a time as a single output according to the selection line inputs. CO2-App (8)  
(ii) Write a Verilog program for 3 to 8 decoder in gate level description. CO2-App (8)

Or

- (b) Design a 4-bit adder in which the carry-out of each full adder is the carry in of the succeeding next most significant full adder using Verilog HDL. CO2-App (16)
12. (a) Explain the n- well process in CMOS fabrication. CO1 – U (16)  
Or  
(b) Explain the basic structure and operating mode of N- MOS Transistor based on the magnitude of  $V_{gs}$ . CO1 – U (16)

 
13. (a) Estimate the minimum delay of the path from A to B in the given Figure and choose transistor sizes to achieve this delay. The initial NAND gate may present a load of  $8\lambda$  of transistor width on the input and the output load is equivalent to  $45\lambda$  of transistor width. How should be the transistors be sized to achieve least delay?. CO3-App (16)



Or

- (b) Determine the relative saturation current of 2- and 3-transistor nMOS and pMOS stacks in a 65 nm process.  $V_{DD} = 1.0$  V and  $V_t = 0.3$  V. Use  $V_c = E_c L = 1.04$  V for nMOS devices and 2.22 V for pMOS devices. CO3-App (16)

 14. (a) Two designs for an 8-input domino AND gate using footed dynamic gates are shown in Figure. One uses four stages of logic with static CMOS inverters. The other uses only two stages by employing a HI-skew NOR gate. Analyze at what range of path electrical efforts are the 2-stage design faster? CO5-Ana (16)



Or

- (b) A Multiplexer has a maximum input capacitance of 16 units on each input it must drive load of 150 units analyze the minimum delay for NAND and Compound solution. CO5-Ana (16)
15. (a) Explain in detail about variable threshold voltage and multiple threshold voltage is infeasible due to technological limitation necessary diagrams. CO1 – U (16)

Or

- (b) Explain the need and demand of low power CMOS logic circuits CO1 – U (16)

