

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code:R2I04

B.E./B.Tech. DEGREE EXAMINATION, APRIL / MAY 2025

Second Semester

CSE (Internet of Things)

R21UIO204- DIGITAL SYSTEM DESIGN

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

1. State De-Morgan's theorem. CO1- U
2. Express the function $Y = A + BC$ in canonical POS. CO2-App
3. Why full adder is efficient than the half adders? Justify. CO3-Ana
4. Determine the Boolean expression for a half adder. CO2-App
5. Write the characteristics table of a D flip flop. CO1- U
6. The clock frequency is 2MHz. How long will it take to serial load the eight shift register? CO2-App
7. How can a race in digital circuits can be avoided? CO2-App
8. What is the most important consideration in making state assignments for asynchronous network? CO1- U
9. How does the architecture of a PAL differ from a PROM? CO3-Ana
10. Define Cache memory. CO1- U

PART – B (5 x 16= 80 Marks)

11. (a) For the given truth table ,write the logical expression in the canonical SOP & POS CO2- App (16)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Or

- (b) Write the minimized Boolean expression for the function using K-map CO2- App (16)


$$F(w,x,y,z) = \sum m(0,1,2,4,5,6,8,9,12,13,14).$$

12. (a) Write a brief note on the following combinational circuits: CO1- U (8)
- (i) Full adder
- (ii) Full subtractor CO1- U (8)

Or

- (b) Explain in detail the BCD Adder. CO1- U (16)

 13. (a) Analyze state reduction if possible after designing a clocked synchronous sequential logic circuit using JK flip flops for the following state diagram. Use state reduction if possible. CO2- App (16)



Or

- (b) Design a synchronous counter using JK flipflops to count the sequence 0,1,2,4,5,6,0,1,2. Use State diagram and state table. CO2- App (16)

14. (a) Write a HDL structural description of a full adder using two half adder and OR Write the simulation waveform CO2- App (16)

Or

- (b) An asynchronous sequential circuit is described by the following excitation and output function: CO2- App (8)
- $$Y = X_1X_2 + (X_1 + X_2)Y,$$

$$Z = Y$$

- (i) Draw the logic diagram of the circuit
- (ii) Derive the transition table, output map and describe the behavior of the circuit CO2- App (8)

15. (a) Differentiate static and dynamic RAM. Draw the circuits of one cell of each and explain its working principle. CO1- U (16)

Or

- (b) Write a detailed notes on : CO1- U (8)
- (i) PAL
- (ii) FPGA CO1- U (8)

