

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: U2E05**

B.E./B.Tech. DEGREE EXAMINATION, MAY 2022

Second Semester

Artificial Intelligence & Data Science

21UAD205- Digital Logic Design

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

1. In which code the successive code characters differ in only one bit position? CO1- R  
(a) gray code (b) excess 3 code  
(c) 8421 code (d) algebraic code
2. How many full adder required to design 4 bit binary parallel adder CO2- R  
(a) 1 (b) 2 (c) 3 (d) 4
3. Which of the following flip-flops is free from the race around the problem? CO1- R  
(a) T flip-flop (b) SR flip-flop (c) Master-Slave Flip-flop (d) flip-flop
4. In synchronous circuit, the present state is determined by CO1- R  
(a) unlocked flip-flops (b) clocked flip-flops (c) flip-flops (d) latches
5. For programmable logic functions, which type of PLD should be used? CO1- U  
(a) PLA (b) PAL (c) CPLD (d) SLD

PART – B (5 x 3= 15 Marks)

6. State and prove Demorgan's theorem CO1- R
7. Differentiate Half and Full adder CO2- U
8. Define Priority encoder with truth table and circuit CO1- R
9. List the basic types of shift registers in terms of data movement. CO1- R

10. Define fundamental mode asynchronous sequential circuit CO1- R
- PART – C (5 x 16= 80 Marks)
11. (a) Determine the SOP and POS forms of  $F = (0, 2, 6, 8, 10, 12, 14, 15)$  using k-map CO3-App (16)
- Or
- (b) Reduce the following equation using Quine McClucky method of minimization CO3-App (16)  
 $F(A, B, C, D) = m(0, 1, 3, 4, 5, 7, 10, 13, 14, 15)$
12. (a) Differentiate full subtractor and full adder and design a full adder using NAND gate alone CO3-App (16)
- Or
- (b) Design a circuit for priority encoder CO3-App (16)
13. (a) Explain the operation of JK flip-flops with suitable diagrams? CO3-App (16)
- Or
- (b) Using SR flip flops, design a parallel counter which counts in the sequence 000,111,101,110,001,010,000 ..... CO3-App (16)
14. (a) Give hazard-free realization for the following Boolean function CO3-App (16)  
 $f(A, B, C, D) = \pi(0, 2, 6, 7, 8, 10, 12)$
- Or
- (b) Give hazard-free realization for the following Boolean function CO3-App (16)  
 $f(A, B, C, D) = \pi(3, 4, 7, 8, 9, 12, 15)$
15. (a) Explain in detail about Static and dynamic RAM with neat diagram? CO3-App (16)
- Or
- (b) Implement the following functions using PLA. CO3-App (16)  
 $F_1(A, B, C) = \Sigma m(1, 2, 4, 6)$   
 $F_2(A, B, C) = \Sigma m(0, 1, 6, 7)$   
 $F_3(A, B, C) = \Sigma m(2, 6)$