

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: U2B05

B.E./B.Tech. DEGREE EXAMINATION, MAY 2022

Second Semester

Biomedical Engineering

21UBM205- Human Anatomy And Physiology

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)


- Ohms law holds true only for _____ circuits CO1- R
(a) Linear (b) Non-linear (c) Unilateral (d) None of the above
- Three equal resistances of 3Ω are connected in star. What is the resistance in one of the arms in an equivalent delta circuit CO2- R
(a) 10Ω (b) 3Ω (c) 9Ω (d) 27Ω
- What is the total reactance of a series RLC circuit at resonance? CO2- R
(a) Equal to X_L (b) Equal to X_C (c) Equal to R (d) Zero
- Which amplifier is used in an electronic multimeter? CO4- R
(a) Wideband amplifier (b) Differential amplifier
(c) Buffer amplifier (d) Power amplifier
- Fuse protection is used for current ratings up to CO5- R
(a) 10 A (b) 20 A (c) 50 A (d) 100 A

PART – B (5 x 3= 15 Marks)

- Define ideal voltage source CO1- U
- Define Norton Theorem CO2- U
- What do you understand by resonance? CO3- U
- List the difference between CT and PT CO4- U
- What is the purpose of earthing? CO5- U


PART – C (5 x 16= 80Marks)

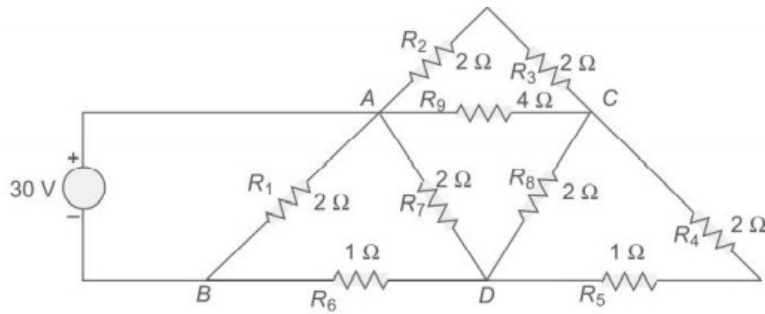11. (a) Determine the current delivered by the source in the circuit shown in Fig CO1-App (16)
in Fig




Or

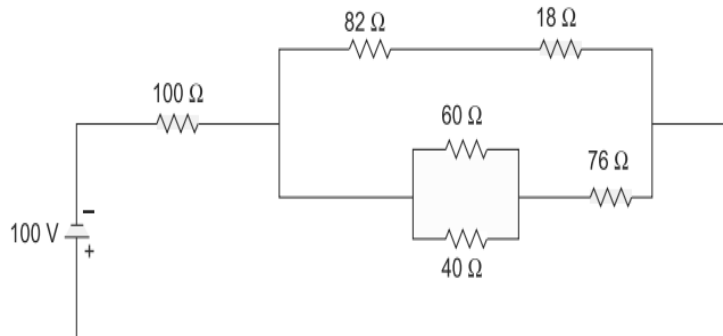- (b) For the circuit shown in Fig., find the total resistance. CO1-App (16)




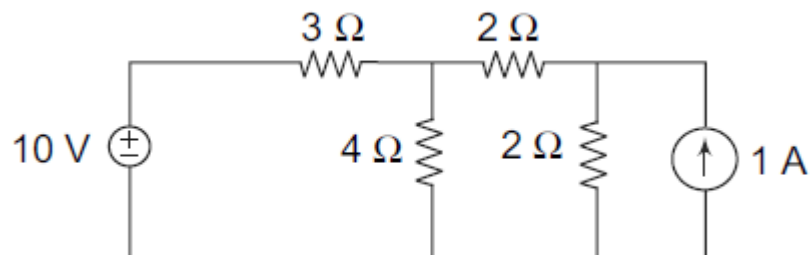12. (a) Calculate the current in the 4 Ω resistor of using the superposition theorem. CO2-App (16)
theorem.



Or

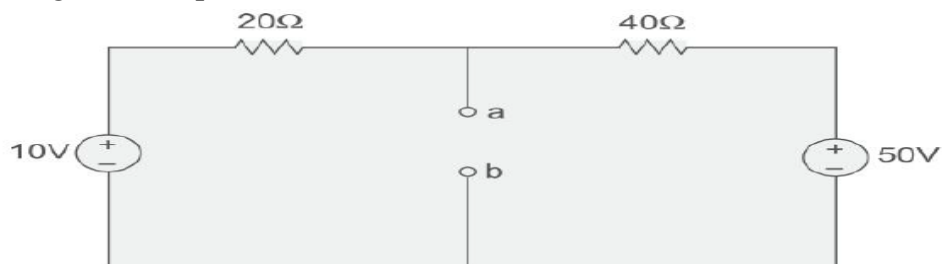
- (b) Find the Thevenin's and Norton's equivalents for the circuit shown in Fig. with respect to terminals ab. CO2-App (16)
in Fig.



13. (a) A series RLC circuit has a quality factor of 5 at 50 rad/s. The current flowing through the circuit at resonance is 10 A and the supply voltage is 100 V. The total impedance of the circuit is 20 V. Find the circuit constants

Or

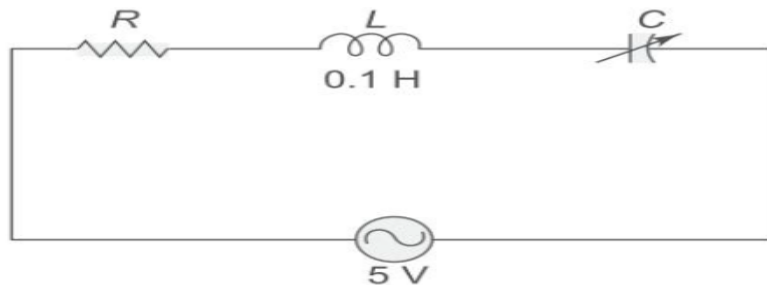- (b) In the circuit shown in Fig. a maximum current of 0.1 A flows through the circuit when the capacitor is at 5 μF with a fixed frequency and a voltage of 5 V. Determine the frequency at which the circuit resonates, the bandwidth, the quality factor Q and the value of resistance at resonant frequency



14. (a) Explain the construction and working principle of PMMC type instrument with necessary diagram

Or

- (b) Elucidate the construction and working principle of an energy meter with necessary circuit arrangement

15. (a) Explain the various methods of electrical wiring system

Or

- (b) What are the basic concepts of household wiring and explain?

