

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 93B05

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2022

Third Semester

Biomedical Engineering

19UBM305 - Semiconductor Devices and Circuits

(Regulation 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

1. Draw V-I characteristics of PN junction diode. CO1 U
2. List the applications of tunnel diode. CO1 U
3. Compare JFET and MOSFET. CO3 Ana
4. Analyze the region of operation for the types of MOSFET. CO3 Ana
5. Define critical frequency(f_c). CO1 U
6. What are the benefits of h-parameter? CO1 U
7. Why RC phase shift oscillator called so? CO3 Ana
8. How does an oscillator differ from an amplifier? CO3 Ana
9. What is Bistable multivibrator? CO1 U
10. What are the applications of clamping circuits? CO1 U

PART – B (5 x 16= 80Marks)

11. (a) Explain the operation of forward biased and reverse biased PN junction Diode CO1- U (16)
Or
(b) Explain in detail about transistor circuit bias. CO1- U (16)
12. (a) Explain in detail the working of JFET .Draw its drain and transfer characteristics. CO1- U (16)
Or
(b) Discuss about the symbol, construction, working and characteristics of UJT and SCR. CO1- U (16)

13. (a) Analyze the single stage CE amplifier using the parameters voltage gain, current gain, input impedance and output admittance. CO3- Ana (16)
- Or
- (b) Analyze the frequency response of single stage transistor amplifier circuit.(BJT or FET) CO3- Ana (16)
14. (a) Draw the circuit diagram of a current series feedback amplifier and derive expressions for voltage gain with and without feedback. CO2- App (16)
- Or
- (b) With a neat sketch explain the working of an RC phase shift oscillator and derive an expression for frequency of oscillation for an RC phase shift oscillator. CO2- App (16)
15. (a) Draw the circuit diagram of Schmitt trigger circuit and explain its operation with waveforms. CO1- U (16)
- Or
- (b) With a neat sketch, explain the working of Bi stable multivibrator CO1- U (16)