

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53402

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2022

Third Semester

Electronics and Communication Engineering

15UEC302 - DIGITAL ELECTRONICS AND DESIGN

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

1. In the eight input possibilities of a 3 input NOR gate, how many of those possibilities will effect in HIGH output? CO1- R
(a) 1 (b) 2 (c) 4 (d) 8
2. A full adder can be constructed out of CO2- R
(a) Two half adders (b) Two half adders and a OR gate
(c) Two half adders and a NOT gate (d) Two half adders and a AND gate
3. The number of states a ring counter with 5 flip flops will have is CO3- R
(a) 5 (b)10 (c) 32 (d) None of the above
4. In Moore models, output is function of only CO4- R
(a) Present state (b) Input state (c) Next state (d) Both (A) and (B)
5. Transistor–transistor logic (TTL) is a class of digital circuits built from CO5- R
(a) JFET (b) Resistors
(c) Bipolar Junction Transistors (d) Bipolar Junction Transistors and Resistors

PART – B (5 x 3= 15Marks)

6. State the drawbacks of K-map method. CO1- R
7. Compare decoder and demultiplexer. CO2- R
8. Differentiate flip-flop from latches. CO3- R

9. Define hazards in asynchronous sequential circuits. CO4- R
10. What is the difference between programmable array logic (PAL) and programmable logic array (PLA)? CO5- R

PART – C (5 x 16= 80 Marks)

11. (a) Simplify the following Boolean function $f(W, X, Y, Z) = \sum m(2, 6, 8, 9, 10, 11, 14, 15)$ using Quine-McClukey tabular method. CO1- App (16)
- Or
- (b) Find a minimal sum of products representation for $F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$ using karnaugh method. Draw the circuit of the minimal expression using only NAND gates. CO1- App (16)
12. (a) Design a 4 bit magnitude comparator and draw its logic diagram. CO2- App (16)
- Or
- (b) Explain the design of BCD adder. CO2- App (16)
13. (a) (i) Draw the logic diagram of a 4-bit universal shift register and explain its operation. CO3- U (8)
- (ii) Explain the working of a Master - slave J-K flip-flop with a neat logic Diagram. CO3- U (8)
- Or
- (b) Design and explain the working of synchronous MOD-6 counter. CO3- U (16)
14. (a) Design a sequence detector that produces an output '1' whenever the non-overlapping sequence 1011 is detected. CO4- U (16)
- Or
- (b) Explain in detail about problems in asynchronous sequential circuits. CO4- U (16)
15. (a) Implement the following two Boolean functions with a programmable logic array (PLA) CO5- U (16)
- $$F_1(A, B, C) = \sum m(0, 1, 3, 4)$$
- $$F_2(A, B, C) = \sum m(1, 2, 3, 4, 5)$$
- Or
- (b) (i) Discuss about FPGA in detail. CO5- U (8)
- (ii) Explain the operation of a TTL 3-input NAND gate with a neat circuit diagram. CO5- U (8)