

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: U2304**

B.E./B.Tech. DEGREE EXAMINATION, MAY 2022

Second Semester

Electrical and Electronics Engineering

21UEE204- Electrical Circuit Analysis

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

1. The resistors values in delta network that is equivalent to a star containing three  $120 \Omega$  resistors is \_\_\_\_\_ CO1- U  
(a)  $360\Omega$  each      (b)  $240\Omega$  each      (c)  $180\Omega$  each      (d)  $120\Omega$  each
2. The form factor of sinusoidal wave form is \_\_\_\_\_ CO2- U  
(a) 1.414      (b) 1.11      (c) 0      (d) 1.5
3. When the power transferred to the load is maximum, the efficiency of power transfer is CO3- U  
(a) 25%.      (b) 100%.      (c) 75%.      (d) 50%
4. In a series resonance circuit, series resonance occurs when? CO4- U  
(a)  $X_L = 1$       (b)  $X_C = 1$       (c)  $X_L = X_C$       (d)  $X_L = - X_C$
5. The value of the time constant in the R-L circuit is? CO5- U  
(a) L/R      (b) R/L      (c) R      (d) L

PART – B (5 x 3= 15 Marks)


6. State Kirchhoff's current law CO1- U
7. A sinusoidal voltage represented by the equation  $100 \sin 503t$ . What is the frequency and time period? CO2- U
8. Write the expression to find the load by using Norton's equivalent circuit CO3- U
9. Write the relation between self and mutual inductance CO4- U

10. What is damping ratio?

CO5- U

PART – C (5 x 16= 80Marks)

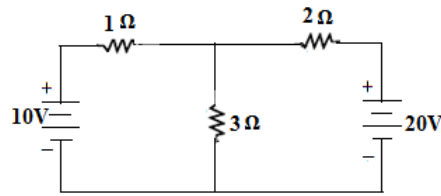11. (a) Find the current through  $3\ \Omega$  resistor in the circuit shown in below fig: CO1-App (16)




Or

- (b) Derive the expression for star connected resistance into delta connected resistance. CO1-Ana (16)
12. (a) Derive an expression for power and power factor of an RC series circuit CO2-Ana (16)


Or

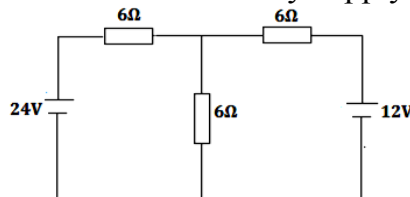- (b) Two impedance  $Z_1 = (6 + j8)\ \Omega$  and  $Z_2 = (3 - j4)\ \Omega$  are connected in parallel. This combination is connected across 230V, 50HZ AC supply. Calculate the current in each branch, total current and total power consumed by the circuit CO2-App (16)
13. (a) compute the current through the 6 ohm load resistance in the following figure shown below by applying upper position theorems CO3-App (16)




Or

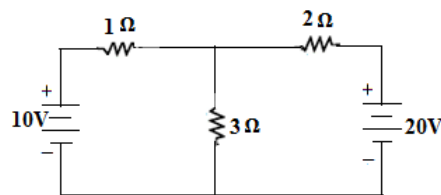- (b) (i) State and explain the procedure for Norton's theorems CO3-Ana (8)
- (ii) In the circuit of figure ,find the current through the batteries by mesh method CO3-App (8)



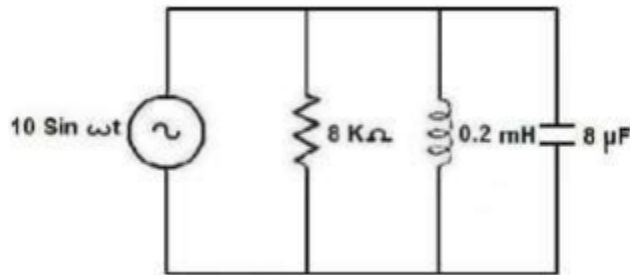14. (a) In the parallel RLC circuit, calculate resonant frequency, bandwidth Q-factor and power dissipated at half power frequencies. CO4-App (16)



Or

- (b) (i) Obtain the expression for resonant frequency, bandwidth and Q-factor for Series R-L-C circuit CO4-U (8)  
(ii) Compare series and parallel resonance. CO4-U (8)
15. (a) Derive an current response of RC series circuit with an excitation of  $V \sin(\omega t)$  CO5-App (16)
- Or
- (b) Derive the transient response of RC series circuit when the switch is closed at  $t=0$  CO5-Ana (16)

