

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 93403**

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2021

Third Semester

Electronics and Communication Engineering

19UEC303 - Circuit Theory

(Regulation 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)


- Ohms law holds true only for ----- circuits CO1- U  
(a) Linear (b) Non-linear (c) Unilateral (d) None
- Superposition theorem is not valid for CO3- R  
(a) voltage responses (b) current responses (c) power responses (d) all the three
- What is the total reactance of a series RLC circuit at resonance? CO4- R  
(a) Equal to  $X_L$  (b) Equal to  $X_C$  (c) Equal to R (d) Zero
- Inductor does not allow sudden changes CO5- R  
(a) in currents (b) in voltages (c) in both (a) and (b) (d) in none of the above
- For a two-port network to be reciprocal, CO6- R  
(a)  $Z_{11}=Z_{22}$  (b)  $y_{21} = y_{12}$  (c)  $h_{21} = - h_{12}$  (d)  $AD - BC = 0$

PART - B (5 x 3= 15 Marks)

- State and explain Kirchhoff's Laws CO1 U
- Explain dual with reference to network. CO3 U
- What do you understand by resonance? CO4 U
- Distinguish between natural and forced response CO5 U
- Define ABCD parameters for a two-port network. CO6 U


PART – C (5 x 16= 80 Marks)

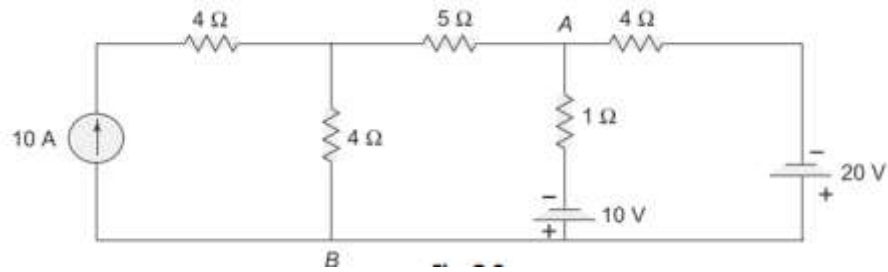11. (a) Find the voltage between A and B of the circuit shown in Fig. by mesh analysis. CO2- App (16)




Or

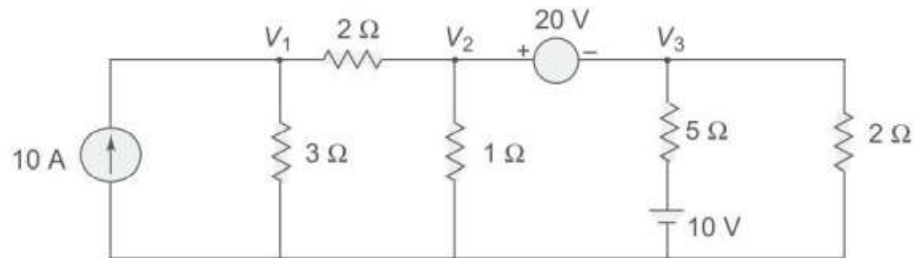- (b) Determine the current in the 5 V resistor for the circuit shown in Fig CO2- App (16)



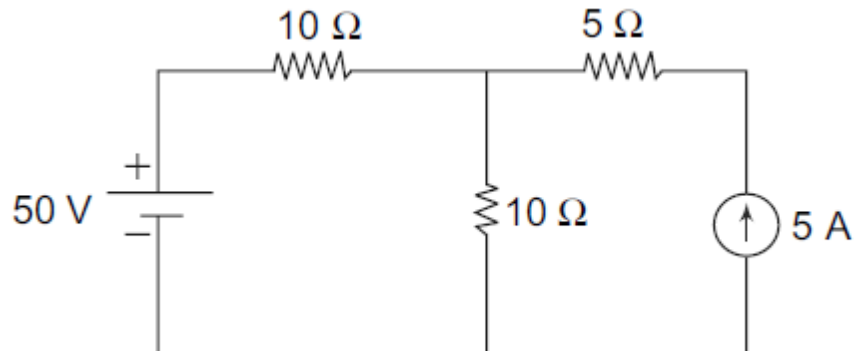
12. (a) Find the current through various branches of the circuit shown in Fig by employing the superposition theorem. CO3- App (16)



Or

(b) Find Thevenin's equivalent circuit for the circuit shown in Fig.

CO3- App (16)

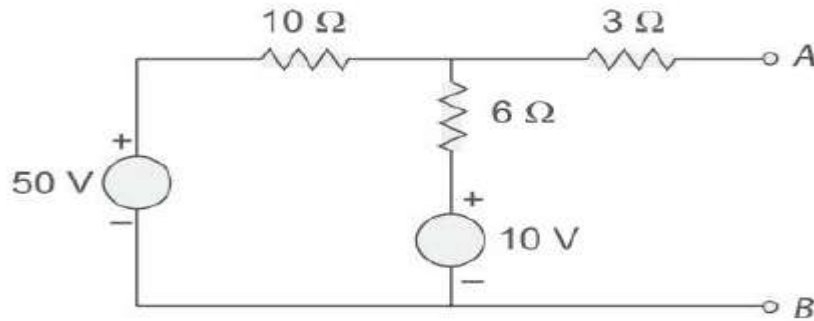


13. (a) A series RLC circuit has a quality factor of 5 at 50 rad/s. The current flowing through the circuit at resonance is 10 A and the supply voltage is 100 V. The total impedance of the circuit is 20 V. Find the circuit constants

CO4- App (16)

Or


(b) In the circuit shown in Fig. a maximum current of 0.1 A flows through the circuit when the capacitor is at 5  $\mu$ F with a fixed frequency and a voltage of 5 V. Determine the frequency at which the circuit resonates, the bandwidth, the quality factor Q and the value of resistance at resonant frequency

CO4- App (16)

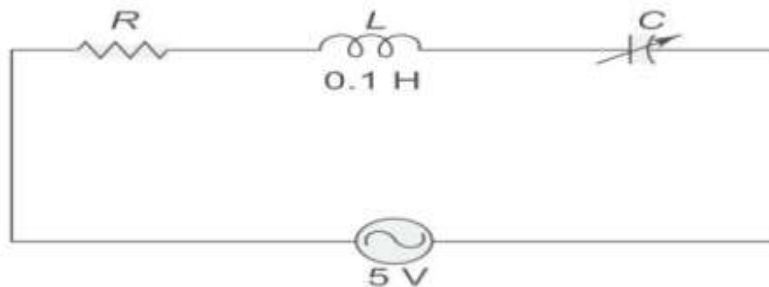


14. (a) The circuit shown in Fig consists of resistance, inductance, and capacitance in series with a 100 V constant source when the switch is closed at  $t = 0$ . Find the current transient.

CO5- App (16)

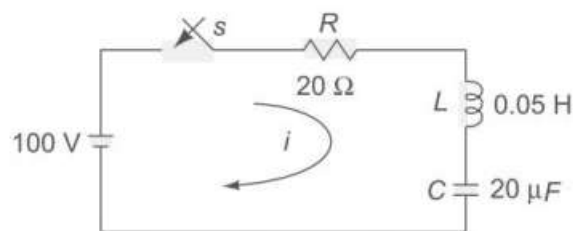

Or

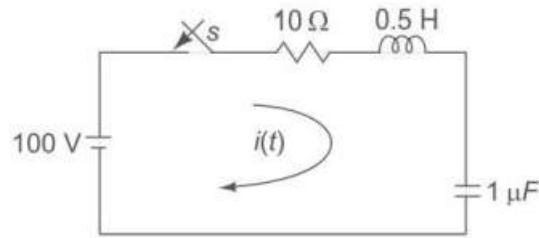- (b) A series RLC circuit shown in Fig, comprising  $R = 10\Omega$ ,  $L = 0.5\text{H}$ , and  $C = 1\mu\text{F}$ , is excited by a constant voltage source of  $100\text{V}$ . Obtain the expression for the current. Assume that the circuit is relaxed initially. CO5- App (16)



15. (a) The impedance parameters of a two-port network are  $Z_{11} = 6\Omega$ ;  $Z_{22} = 4\Omega$ ;  $Z_{12} = Z_{21} = 3\Omega$ . Compute the Y-parameters and ABCD- parameters and write the describing equations CO6- App (16)

Or

- (b) Determine the Z parameters of the network shown in fig CO6- App (16)

