

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 45303

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2021

Fifth Semester

Electrical and Electronics Engineering

14UEE503 - POWER SYSTEM ANALYSIS

(Regulation 2014)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. What will be the per unit impedance of a synchronous motor having a rating of 100 kVA, 13.2 kV and having a reactance of $75 \Omega / \text{ph}$?
(a) 0.043 pu (b) 0.057 pu (c) 0.036 pu (d) 0.298 pu
2. To control which among the following is the regulating transformer used in a power system?
(a) Power flows (b) Frequency (c) Voltage (d) Power factor
3. What is the value of acceleration factor used in the GS method?
(a) 2.3 – 2.7 (b) 1.6 – 2.0 (c) 1.2 – 1.5 (d) 2.4 – 2.9
4. Initially what will be the voltage at all the PQ buses for solving the load flow problem using NR method.
(a) $V_i = 1 \angle 90^\circ$ (b) $V_i = 1 \angle 0^\circ$ (c) $V_i = 1 \angle 180^\circ$ (d) $V_i = 1 \angle 45^\circ$
5. Which among these is the most severe fault?
(a) Single line to ground fault (b) Double line to ground fault
(c) Line to line fault (d) Symmetrical fault

(delta / star) : 30 MVA, 11/220 kV, $X = 15\%$

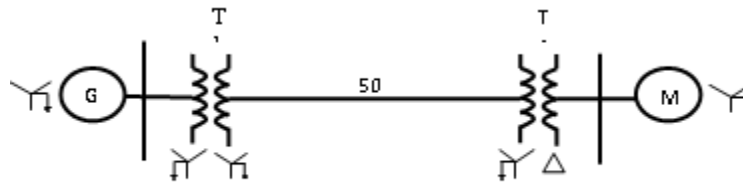


Figure 1

Or

(b) Explain the modelling of generator, load, transmission line and transformer for power flow, short circuit and stability studies. (16)

17. (a) Explain the algorithm of Gauss Seidal method for the load flow problem with a neat flow chart and relevant equations. (16)

Or

(b) Clearly the algorithmic steps for solving load flow equations using Newton – Raphson method (polar form) when the system contains all types of buses. Assume that the generators at the P-V buses have adequate Q- limits. (16)

18. (a) A 11 kV, 100 MVA alternator having a sub-transient reactance of 0.25 pu is supplying to a 50 MVA motor having a sub-transient reactance of 0.2 pu through a transmission line. The line reactance is 0.05 pu on a base of 100 MVA. The motor is drawing 40 MW at 0.8 pf. leading with a terminal voltage of 10.95 kV when a 3-phase fault occurs at the generator terminals. Calculate the total current in generator and motor under fault conditions. (16)

Or

(b) Explain the step by step procedure of symmetrical fault analysis using bus impedance matrix with neat algorithm. (16)

19. (a) (i) What are the assumptions to be made in short circuit studies? (4)

(ii) Deduce and draw the sequence network for a line to line fault at the terminals of an unloaded generator. (12)


Or

(b) Derive the relationship to determine the fault current for a single line to ground fault on an unloaded generator. Draw an equivalent network showing the interconnection of sequence of networks to simulate single line to ground fault. (16)

20. (a) (i) Derive swing equation of synchronous machine. (10)
 (ii) Distinguish between steady state, transient and dynamic stability. (6)

Or

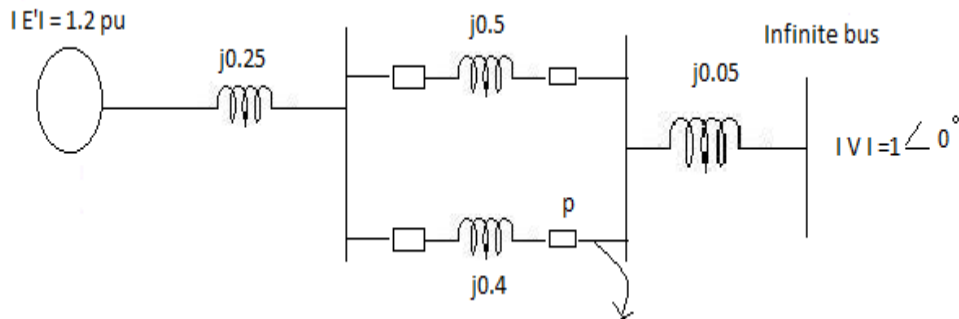(b) For the given system a three phase fault occurs at the point P. Find the critical clearing angle for clearing the fault with simultaneous opening of the breakers 1 and 2. The reactance values of various components are indicated on the diagram. The generator is delivering 1.0 pu power at the instant preceding the fault.



(16)