

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 42307

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2021

Second Semester

Electrical and Electronics Engineering

14UEE207- ELECTRIC CIRCUITS

(Regulation 2014)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions.

PART A - (10 x 1 = 10 Marks)

1. If a resistor to carry 1 A of current to handle 100 W of power, estimate the value of resistance.
Assume that voltage can be adjusted to any required value.
(a) 50 Ω (b) 100 Ω (c) 10 Ω (d) 1 Ω
2. A 100 Ω resistor is connected across the terminals of a 9 V battery. What is the power dissipation in the resistor?
(a) 9 W (b) 0.9 W (c) 0.19 W (d) 0.81 W
3. Three equal resistances of 9 Ω are connected in delta. What is the resistance in one of the arms in an equivalent star circuit?
(a) 3 Ω (b) 9 Ω (c) 1 Ω (d) 27 Ω
4. Maximum power is transferred to load, when the load resistance is
(a) equal to half of the source resistance (b) equal to source resistance
(c) equal to zero (d) equal to twice the source resistance
5. In a series RLC circuit, if C is increased, the resonant frequency
(a) Increases (b) Decreases (c) Remains the same (d) Becomes zero
6. The admittance and impedance of the following kind of network have the same properties
(a) LC (b) RL (c) RC (d) RLC


7. In a series parallel circuit, any two resistances in the same current path must be in
 (a) series with each other (b) parallel with each other
 (c) series with the voltage source (d) parallel with the voltage source
8. An RL circuit has $R = 2 \Omega$ and $L = 4 H$. The time constant is
 (a) $4s$ (b) $0.5s$ (c) $8s$ (d) $2s$
9. In a Y-Y system, a line voltage of $220 V$ produces a phase voltage of
 (a) $381 V$ (b) $156 V$ (c) $127 V$ (d) $22 V$
10. In the measurement of 3 phase power by two Wattmeter method, if the two Wattmeter readings are equal and have same sign, the power factor of the circuit is
 (a) unity (b) zero (c) 0.8 leading (d) 0.8 lagging

PART - B (5 x 2 = 10 Marks)

11. Two coils connected in series have a resistance of 18Ω and when connected in parallel of 4Ω . Evaluate the value of resistance of two coils.
12. State the Thevenin's theorem.
13. Point out the relation between self and mutual inductance.
14. Categorize the different types damping conditions occurred in RLC transient circuits.
15. Two inductively coupled coils have self inductances $L1 = 50 mH$ and $L2 = 200 mH$. If the coefficient of coupling is 0.5 , compute the value of mutual inductance between the coils.


PART - C (5 x 16 = 80 Marks)

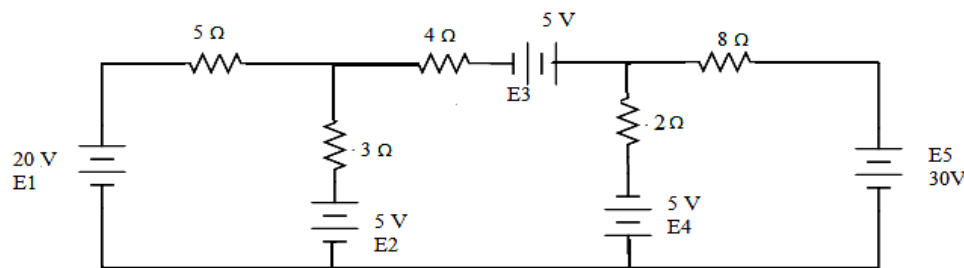16. (a) Determine the current supplied by each battery in the circuit shown in figure using mesh analysis. (16)




Or

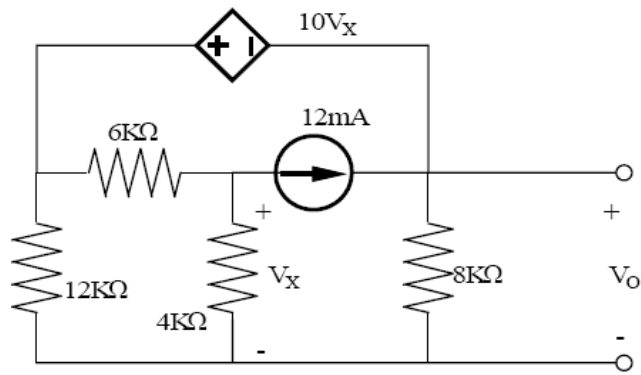- (b) Calculate V_o from the following circuit shown below using mesh analysis. (16)




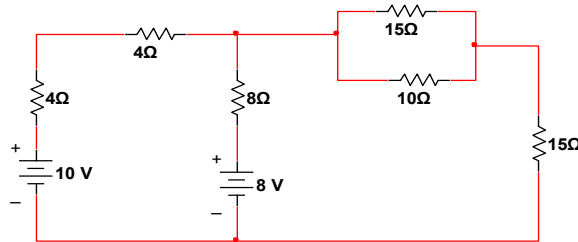17. (a) Calculate the current in 10Ω resistor of the network shown below using superposition theorem. (16)



Or

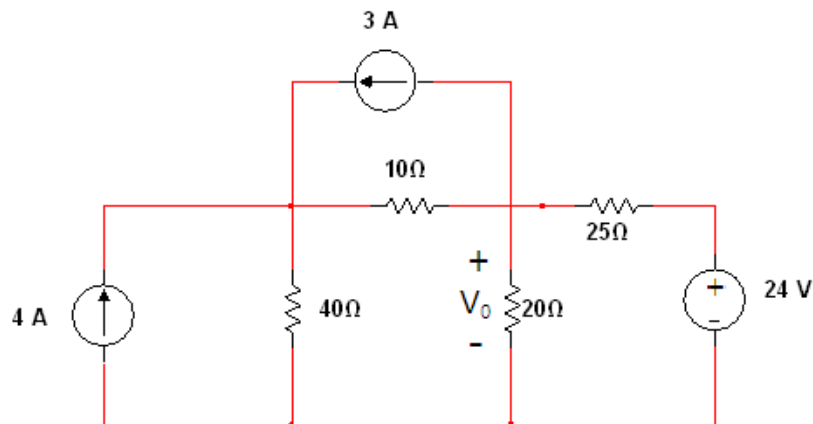- (b) Calculate the voltage V_o for the given circuit below. (16)



18. (a) For a two-branch parallel circuit $R_L = 15 \Omega$, $R_C = 30 \Omega$, $X_C = 30 \Omega$, $E = 120 V$ and $f = 60 Hz$. For the condition of resonance, calculate (1) the two values of L and (2) the two values of total current. (16)

Or

- (b) (i) A coil of resistance 3Ω and inductance $100 mH$ is connected in series with a $100 \mu F$ capacitor across a $220 V$, $50 Hz$ supply. Calculate (1) Impedance of the circuit in polar form (2) the current (3) power factor and (4) voltage across each element. (16)

19. (a) Derive the expression for the current $i(t)$ in the series RC circuit: (a) with initial conditions (b) with relaxed initial conditions for a step input excitation, using Laplace transform technique. (16)

Or

- (b) Find the Y parameters for the RC ladder network shown in Fig.8. (16)

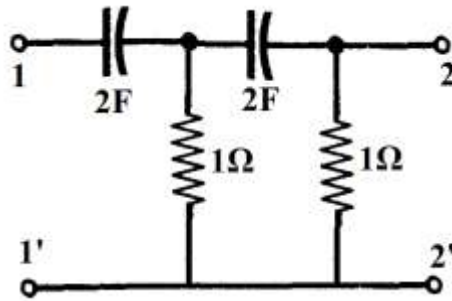


Fig.8

20. (a) With a neat circuit and phasor diagram explain the three phase power and power factor measurement by two Wattmeter method. (16)

Or

- (b) Explain in detail the phasor diagrams of the voltages and currents of a three phase unbalanced circuit. (16)