Reg. No. :										
------------	--	--	--	--	--	--	--	--	--	--

Maximum: 100 Marks

Question Paper Code: 36301

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2021

Sixth Semester

Electrical and Electronics Engineering

01UEE601 - ELECTRIC DRIVES AND CONTROL

(Regulation 2013)

Duration: Three hours

Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

- 1. What are the three modes of operation of an electrical drive?
- 2. Drive the equations governing motor load dynamics.
- 3. What is CLC in chopper fed drive?
- 4. What is time ratio control?
- 5. List out the different methods of speed control of 3 phase induction motors.
- 6. What are the merits and demerits of stator voltage control?
- 7. What is meant by power factor control?
- 8. What is self control of synchronous motor drive?
- 9. Name any two simulation packages used for drive systems.
- 10. Compare VSI fed drives with CSI fed drives.

PART - B (
$$5 \times 16 = 80$$
 Marks)

11. (a) Explain the multi-quadrant operation of the electric drive with the help of Hoist Load. (16)

- (b) Derive the mathematical condition to obtain steady state stability of equilibrium point. (16)
- 12. (a) Explain in detail the operation and steady state analysis of single phase fully controlled converter fed separately excited dc motor drive in continuous and discontinuous conduction mode. (16)

Or

- (b) Explain the operation of four quadrant chopper control in dc drives. (16)
- 13. (a) Explain about variable frequency control in induction motor drives. (16)

Or

- (b) Explain about V/ F control in Induction motor. (16)
- 14. (a) With necessary diagrams explain the vector control of induction motor drives. (16)

Or

- (b) Explain self-control of synchronous motor drive operated with constant margin angle control. (16)
- 15. (a) Derive the transfer function of a separately excited DC motor load converter system. (16)

Or

(b) Explain closed loop operation of armature voltage control method with field weakening mode control in detail. (16)