

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 93303

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2021

Third Semester

Electrical and Electronics Engineering

19UEE304 - Analog Electronics

(Regulation 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. If the positive terminal of the battery is connected to the anode of the diode, then it is known as CO1- R
(a) Forward biased (b) Reverse biased (c) Equilibrium (d) Schottky barrier
2. The number of pn junctions in a BJT is/are CO1- R
(a) 1 (b) 2 (c) 3 (d) 4
3. The total emitter current (IE) is given by _____ CO2-App
(a) $IE = I_{pE} * I_{nE}$ (b) $IE = I_{pE} - I_{nE}$ (c) $IE = I_{pE} / I_{nE}$ (d) $IE = I_{pE} + I_{nE}$
4. A transistor has an IC of 100Ma and IB of 0.5Ma. What is the value of α_{dc} ? CO2-App
(a) 0.565 (b) 0.754 (c) 1.24 (d) 0.995
5. Which of the following is not a terminal for the operational amplifier? CO3- U
(a) Inverting terminal (b) Non-inverting terminal
(c) Output terminal (d) None of the mentioned
6. What are the units of slew rate? CO3- U
(a) Second/Volt (b) Volt/second (c) It is a ratio, no units (d) Ohm/second
7. A phase shift oscillator is designed to oscillate at 155Hz. Determine the value of R_f . (Take $C=0.30\mu F$) CO4- App
(a) 399Ω (b) $3.98M\Omega$ (c) $13.9K\omega$ (d) $403K\omega$

8. Calculate the frequency of oscillation for RC phase shift oscillator having the value of R and C as 35Ω and $3.7\mu\text{F}$ respectively. CO5- App
- (a) 1230 Hz (b) 204 Hz (c) 502Hz (d) 673 Hz
9. Determine the time period of a monostable 555 multivibrator CO5- App
- (a) $T = 0.33RC$ (b) $T = 1.1RC$ (c) $T = 3RC$ (d) $T = RC$
10. A monostable multivibrator has $R = 120\text{K}\Omega$ and the time delay $T = 1000\text{ms}$, CO5- App
calculate the value of C?
- (a) $0.9\mu\text{F}$ (b) $1.32\mu\text{F}$ (c) $7.5\mu\text{F}$ (d) $2.49\mu\text{F}$

PART – B (5 x 2= 10 Marks)


11. Draw the VI characteristics of PN junction diode. CO1-U
12. A transistor is connected in CE configuration. Collector supply voltage $V_{cc}=10\text{V}$, $R_L=800\Omega$, voltage drop across $R_L=0.8\text{V}$, $\alpha=0.96$. What is base current? CO2-App
13. List out the applications of Integrator and Differentiator CO3-U
14. Draw a circuit for converting a square wave into a series of positive pulses. CO4-App
15. How VCO differ from oscillator? CO4-U

PART – C (5 x 16= 80Marks)

16. (a) Derive the construction of PN junction diode. Explain the forward and reverse characteristic of PN junction diode and obtain its VI characteristic curve. CO1-U (16)
- Or
- (b) Explain the construction and principle of operation of depletion MOSFET with suitable diagram. CO2-App (16)
17. (a) Draw the voltage divider bias circuit and derive an expression for its stability factor. CO2- App (16)
- Or
- (b) Draw the circuit diagram of an emitter-coupled differential amplifier and explain the operation. CO2- U (16)
18. (a) Draw and explain the operation of an ac voltage follower having very high input resistance. CO3- U (16)

Or

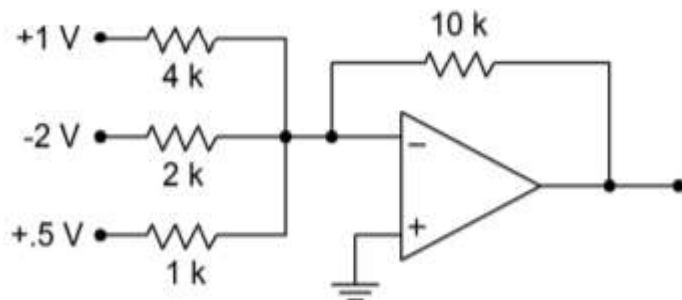- (b) What is the output of the summing amplifier in figure below, with the given DC input voltages? CO3- Ana (16)



19. (a) Draw the circuit of a Wien Bridge oscillator and derive an expression for its frequency of oscillation. CO4- App (16)

Or

- (b) Explain how a comparator can be used as a zero crossing detector CO4- App (16)

20. (a) Design a symmetrical square waveform generator of 10kHz using 555 timer. CO5- C (16)

Or

- (b) Design a monostable multivibrator with trigger pulse shaping which will drive a LED on for 0.5 second each time is pulsed. CO4- C (16)

