

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: U2425

B.E./B.Tech. DEGREE EXAMINATION, NOV 2022

Second Semester

Computer Science and Business Systems

21UEC225- Principles Of Electronics Engineering

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

1. The efficiency of half wave rectifier is? CO1- U
(a) 100% (b) 90% (c) 81.2% (d) 42.5%
2. In an NPN transistor, the arrow is pointed towards _____ CO1- U
(a) the collector (b) the base (c) depends on the configuration (d) the emitter
3. The SI Units of the Process transconductance Parameter (k') is CO1- R
(a) V^2/A (b) A/V^2 (c) V/A (d) A/V
4. Which of the following gate is called universal gate? CO2- U
(a) AND (b) OR (c) XOR (d) NAND
5. The truth table for an S-R flip-flop has how many VALID entries? CO2- U
(a) 1 (b) 2 (c) 3 (d) 4

PART – B (5 x 3= 15 Marks)

6. Calculate the ripple factor of full wave rectifier if $V_m=20V$ CO3- App
7. List out the transistor H-parameters CO1- U
8. Difference between BJT and JFET. CO1- U
9. Implement the half adder using OR gate CO4- App
10. Differentiate SIPO and PIPO ? CO2- U

PART – C (5 x 16= 80Marks)

11. (a) Design a half wave rectifier using PN diode and calculate ripple factor and efficiency CO3-App (16)
- Or
- (b) Compare Half wave, Full wave and Bridge rectifier. CO6-Ana (16)
12. (a) Analyze impedance, admittance and gain of transistors to design amplifier with suitable configuration CO6-Ana (16)
- Or
- (b) Relate CB, CC and CE configuration to find current amplification factor with suitable expression CO6-Ana (16)
13. (a) Explain the construction, working and operating characteristics of P-channel JFET with relevant diagrams. CO1-U (16)
- Or
- (b) Explain the principle of operation of enhancement P-channel MOSFET and draw its drain characteristics. CO1-U (16)
14. (a) Design a binary-to-gray code converter and gray to binary code converter similar to basic ROM Structure CO4-App (16)
- Or
- (b) Design a binary-to- BCD converter and BCD to binary code converter similar to basic ROM Structure CO4-App (16)
15. (a) Design PISO and PIPO shift register using D flipflop. CO4-App (16)
- Or
- (b) Analyze the use of up /down counter in radar applications CO5-Ana (16)