

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: U2304

B.E./B.Tech. DEGREE EXAMINATION, NOV 2022

Second Semester

Electrical and Electronics Engineering

21UEE204- Electrical Circuit Analysis

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

- Which among the following is true about ohm's law? CO1- U
(a) $I \propto V$ (b) $I = V/R$ (c) $V = IR$ (d) All of the above
- The form factor of sinusoidal wave form is ____ CO2- U
(a) 1.414 (b) 1.11 (c) 0 (d) 1.5
- When the power transferred to the load is maximum, the efficiency of power transfer is CO3- U
(a) 25%. (b) 100%. (c) 75%. (d) 50%
- In a series resonance circuit, series resonance occurs when? CO4- U
(a) $X_L = 1$ (b) $X_C = 1$ (c) $X_L = X_C$ (d) $X_L = - X_C$
- The time constant of an R-C circuit is? CO5- U
(a) RC (b) R/C (c) R (d) C

PART – B (5 x 3= 15 Marks)


- Two resistors of 4Ω and 6Ω are connected in parallel. If the total current is 30A. Find the current through each resistor. CO1- U
- A sinusoidal voltage represented by the equation $100 \sin 503t$. What is the frequency and time period? CO2- U
- Write the expression to find the load by using Norton's equivalent circuit CO3- U
- Write the relation between self and mutual inductance CO4- U

10. What is damping ratio?

CO5- U


PART – C (5 x 16= 80Marks)

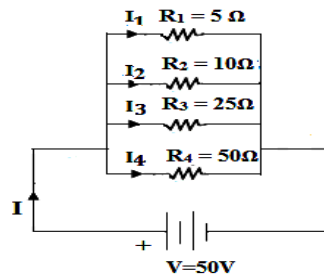11. (a) In the circuit shown below, find the total resistance and the current through each branch. CO1-App (16)



Or

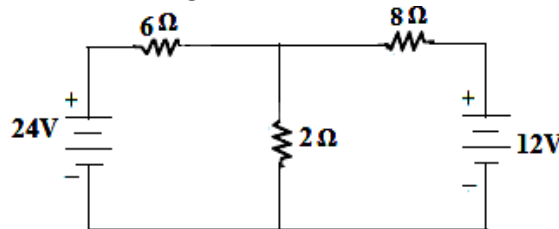- (b) By using Kirchoff's law, find the current supplied by the batteries and the current through 2 Ω resistors for the circuit below CO1-App (16)




12. (a) Derive an expression for power and power factor of an RC series circuit CO2-Ana (16)

Or


- (b) Two impedance $Z_1 = (6 + j8) \Omega$ and $Z_2 = (3 - j4) \Omega$ are connected in parallel. This combination is connected across 230V, 50HZ AC supply. Calculate the current in each branch, total current and total power consumed by the circuit CO2-App (16)

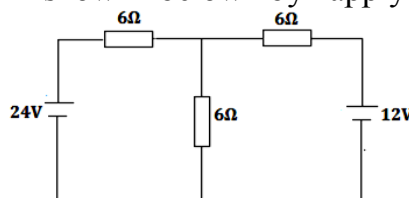13. (a) compute the current through the 6 ohm load resistance in the following figure shown below by applying upper position theorems CO3-App (16)




Or

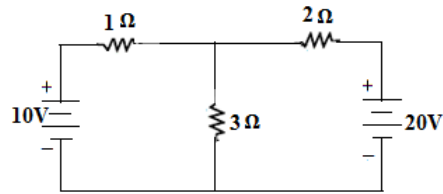- (b) (i) State and explain the procedure for Norton's theorems CO3-Ana (8)
(ii) In the circuit of figure, find the current through the batteries by mesh method CO3-App (8)



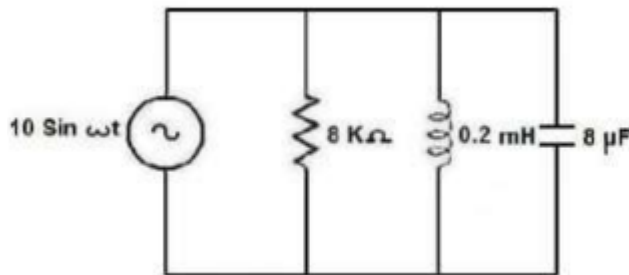14. (a) In the parallel RLC circuit, calculate resonant frequency, bandwidth Q-factor and power dissipated at half power frequencies. CO4-App (16)



Or

- (b) (i) Obtain the expression for resonant frequency, bandwidth and Q-factor for Series R-L-C circuit CO4-U (8)
(ii) Compare series and parallel resonance. CO4-U (8)
15. (a) Derive the step response of RL and RLC circuits. Compare their performance CO5-Ana (16)
- Or
- (b) Derive the transient response of RC series circuit when the switch is closed at $t=0$ CO5-Ana (16)

