

**A**

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 93303**

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2022

Third Semester

Electrical and Electronics Engineering

19UEE304 - Analog Electronics

(Regulation 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- For low value of  $V_{DS}$ , the JFET behaves like a \_\_\_\_\_ CO1- U  
(a) Voltage Variable Resistor (b) Constant Voltage Device  
(c) Amplifier (d) Switch
- The number of pn junctions in a BJT is/are CO1- U  
(a) 1 (b) 2 (c) 3 (d) 4
- The total emitter current ( $I_E$ ) is given by \_\_\_\_\_ CO2-App  
(a)  $I_E = I_{pE} * I_{nE}$  (b)  $I_E = I_{pE} - I_{nE}$  (c)  $I_E = I_{pE} / I_{nE}$  (d)  $I_E = I_{pE} + I_{nE}$
- A transistor has an  $I_C$  of 100Ma and  $I_B$  of 0.5Ma. What is the value of  $\alpha_{dc}$ ? CO2-App  
(a) 0.565 (b) 0.754 (c) 1.24 (d) 0.995
- Which of the following is not a terminal for the operational amplifier? CO3- U  
(a) Inverting terminal (b) Non-inverting terminal  
(c) Output terminal (d) None of the mentioned
- What are the units of slew rate? CO3- U  
(a) Second/Volt (b) Volt/second (c) It is a ratio, no units (d) Ohm/second
- A phase shift oscillator is designed to oscillate at 155Hz. Determine the CO4- App  
value of  $R_f$ . (Take  $C=0.30\mu F$ )  
(a) 399 $\Omega$  (b) 3.98M $\Omega$  (c) 13.9K $\omega$  (d) 403K $\omega$

8. Calculate the frequency of oscillation for RC phase shift oscillator having the value of R and C as  $35\Omega$  and  $3.7\mu\text{F}$  respectively. CO5- App
- (a) 1230 Hz                      (b) 204 Hz                      (c) 502Hz                      (d) 673 Hz
9. Determine the time period of a monostable 555 multivibrator CO5- App
- (a)  $T = 0.33RC$                       (b)  $T = 1.1RC$                       (c)  $T = 3RC$                       (d)  $T = RC$
10. Analog phase detector is often referred as CO5- App
- (a) Full wave detector                      (b) Half wave detector
- (c) Rectifier wave detector                      (d) None of the above

PART – B (5 x 2= 10 Marks)


11. Differentiate between intrinsic and extrinsic semiconductor CO1-U
12. A transistor is connected in CE configuration. Collector supply voltage  $V_{cc}=10\text{V}$ ,  $R_L=800\Omega$ , voltage drop across  $R_L=0.8\text{V}$ ,  $\alpha=0.96$ . What is base current? CO2-App
13. List out the applications of Integrator and Differentiator CO3-U
14. Draw a circuit for converting a square wave into a series of positive pulses. CO4-App
15. How VCO differ from oscillator? CO4-U

PART – C (5 x 16= 80Marks)

16. (a) Derive the construction of Zener diode. Explain the forward and reverse characteristic of Zener diode and obtain its VI characteristic curve. CO1-U (16)
- Or
- (b) Explain the construction and principle of operation of depletion MOSFET with suitable diagram. CO2-App (16)
17. (a) Draw the voltage divider bias circuit and derive an expression for its stability factor. CO2- App (16)
- Or
- (b) Draw the circuit diagram of an emitter-coupled differential amplifier and explain the operation. CO2- U (16)
18. (a) Draw and explain the operation of an ac voltage follower having very high input resistance. CO3- U (16)

Or

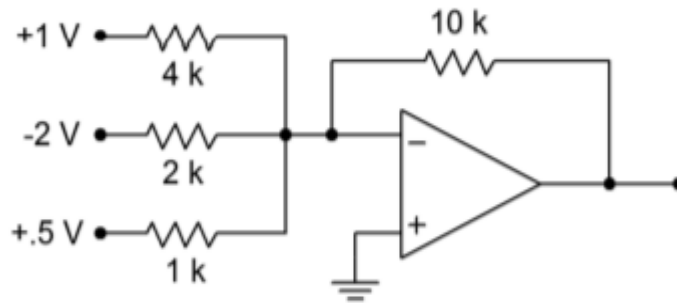- (b) What is the output of the summing amplifier in figure below, with the given DC input voltages? CO3- Ana (16)



19. (a) Draw the circuit of a Wien Bridge oscillator and derive an expression for its frequency of oscillation. CO4- App (16)

Or

- (b) Explain how a comparator can be used as a zero crossing detector CO4- App (16)
20. (a) Explain the functional block diagram of 555 timer. CO5- U (16)

Or

- (b) Design a monostable multivibrator with trigger pulse shaping which will drive a LED on for 0.5 second each time is pulsed. CO4- C (16)



