

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: U2B05

B.E./B.Tech. DEGREE EXAMINATION, NOV 2022

Second Semester

Biomedical Engineering

21UBM205- Electrical Circuits and Measurements

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

1. The duality property is CO1- R
(a) competitive (b) mutual (c) associative (d) linear
2. Three equal resistances of 3Ω are connected in star. What is the resistance in one of the arms in an equivalent delta circuit CO2- R
(a) 10Ω (b) 3Ω (c) 9Ω (d) 27Ω
3. What is the total reactance of a series RLC circuit at resonance? CO2- R
(a) Equal to X_L (b) Equal to X_C (c) Equal to R (d) Zero
4. Which amplifier is used in an electronic multimeter ? CO4- R
(a) Wideband amplifier (b) Differential amplifier
(c) Buffer amplifier (d) Power amplifier
5. Fuse protection is used for current ratings up to CO5- R
(a) 10 A (b) 20 A (c) 50 A (d) 100 A

PART – B (5 x 3= 15 Marks)


6. Explain the source-transformation technique CO1- U
7. Define reciprocity theorem? CO2- U
8. What do you understand by resonance? CO3- U
9. List the difference between CT and PT CO4- U

10. What is the purpose of earthing ?

CO5- U


PART – C (5 x 16= 80Marks)

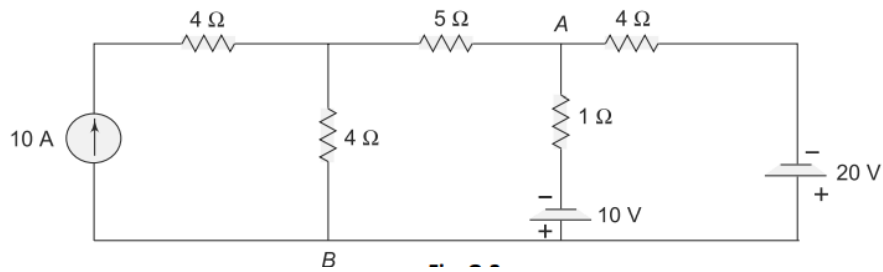11. (a) Find the voltage between A and B of the circuit shown in Fig. by mesh analysis. CO1-App (16)




Or

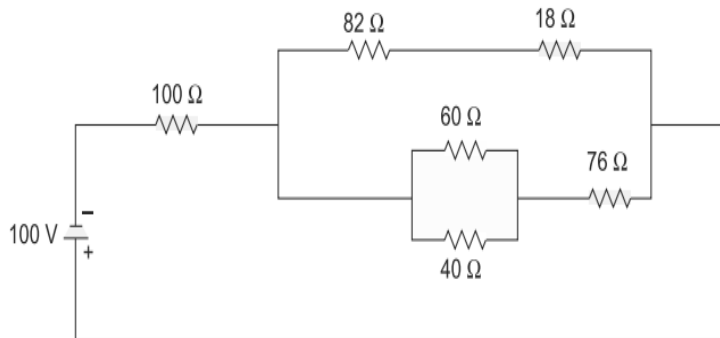(b) For the circuit shown in Fig., find the total resistance. CO1-App (16)




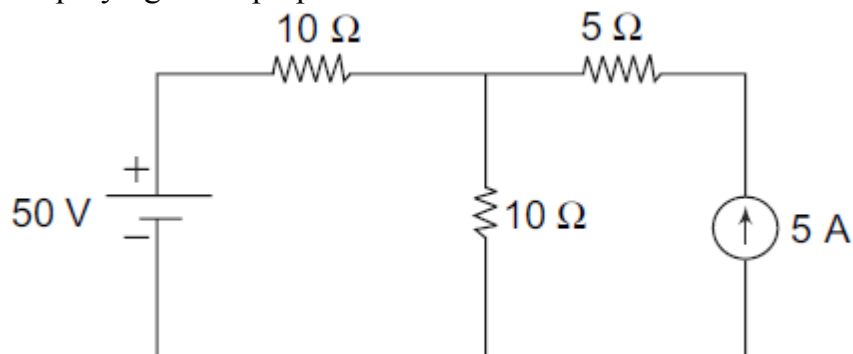12. (a) Find the current through various branches of the circuit shown in Fig by employing the superposition theorem. CO2-App (16)



Or

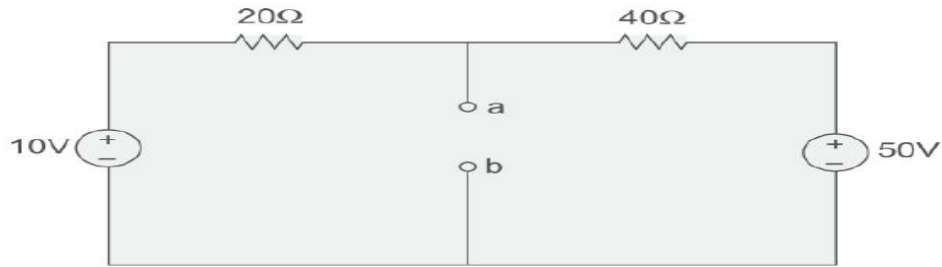
- (b) Find the Thevenin's and Norton's equivalents for the circuit shown in Fig. with respect to terminals ab. CO2-App (16)



13. (a) A series RLC circuit consists of a 50 V resistance, 0.2 H inductance, and 10 μ F capacitor with an applied voltage of 20 V. Determine the resonant frequency. Find the Q-factor of the circuit. Compute the lower and upper frequency limits and also find the bandwidth of the circuit. CO3-App (16)

Or

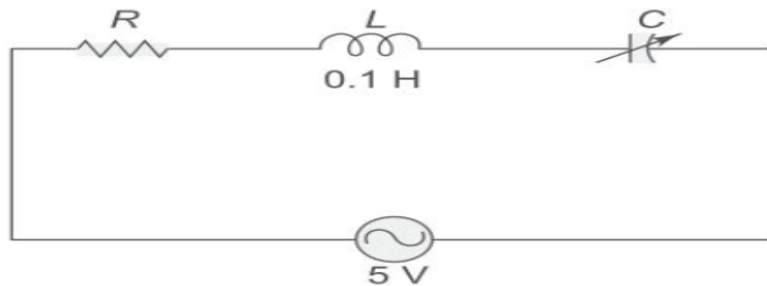- (b) In the circuit shown in Fig. a maximum current of 0.1 A flows through the circuit when the capacitor is at 5 μ F with a fixed frequency and a voltage of 5 V. Determine the frequency at which the circuit resonates, the bandwidth, the quality factor Q and the value of resistance at resonant frequency CO3-App (16)



14. (a) Draw and explain the working principle of attraction type, repulsion type moving iron instrument CO4-U (16)

Or

- (b) Elucidate the construction and working principle of an energy meter with necessary circuit arrangement CO4-U (16)

15. (a) Explain the different cable and wire types with its application CO5-U (16)

Or

- (b) What are the basic concepts of household wiring and explain? CO5-U (16)

