

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: U2205**

B.E./B.Tech. DEGREE EXAMINATION, NOV 2022

Second Semester

Computer Science and Engineering

21UCS205- Digital Electronics

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

1. If  $A=1$  and  $B=0$  then  $A'+B'$  = \_\_\_\_\_ CO1- U  
(a) 0 (b) 1 (c) 2 (d) 3
2. A combinational circuit is one where the output at any time depends only on the \_\_\_\_\_ combination of inputs CO2- U  
(a) Present (b) Finite (c) In-finite (d) Continious
3. In the case of a J-K flip-flop with active \_\_\_\_\_ inputs, the output of the flip-flop toggles CO3- U  
(a) High (b) Low (c) Half (d) Parcials
4. The SR latch consists of \_\_\_\_\_ CO4- U  
(a) 1 input (b) 2 input (c) 3 input (d) 4 input
5. Which type of device FPGA are? CO5- U  
(a) SLD (b) SRAM (c) EPROM (d) PLD

PART – B (5 x 3= 15Marks)

6. What is Boolean algebra? CO1- U
7. Define multiplexer CO2- U
8. What is a master-slave flip-flop? CO3- U
9. What are the steps for the design of asynchronous sequential circuit? CO4- U
10. Define Static RAM and dynamic RAM. CO5- U

PART – C (5 x 16= 80Marks)

11. (a) Simplify  $F(A,B,C)=\Sigma(0,1,2,3,7)$  in sum of products and product of sum using K-map. CO1-App (16)
- Or
- (b) Express the following function in a simplified manner using K map technic  $F(X,Y,Z)=\Sigma(0,1,2,6,7)$ . CO1-App (16)
12. (a) Design priority encoder with input  $Cin(X, Y)$  and draw the logic diagram? CO2-App (16)
- Or
- (b) Design a logic circuit that accepts a 4-bit binary code and converts it to 4-bit Gray code with input  $(B3,B2,B1,B0)$  and output  $(G3,G2,G1,G0)$ ? CO2-App (16)
13. (a) Analyze the operation of JK flip-flops with suitable diagrams? CO3-Ana (16)
- Or
- (b) Construct a clocked SR flip-flop with neat diagram and also discuss its performances? CO3-App (16)
14. (a) Explain in detail about Hazards and its types with example? CO4-App (16)
- Or
- (b) Explain in detail about races and types of races with suitable example? CO4-App (16)
15. (a) Implementation of Combinational Logic Circuit using PROM? Using PROM realize the following expression  
 $F1(A, B, C) = \Sigma m(0, 1, 3, 5, 7)$   
 $F2(A, B, C) = \Sigma m(1, 2, 5, 6)$  CO5-App (16)
- Or
- (b) Implement the following functions using PLA. CO5-App (16)  
 $F1(A, B, C) = \Sigma m(1, 2, 4, 6)$   
 $F2(A, B, C) = \Sigma m(0, 1, 6, 7)$   
 $F3(A, B, C) = \Sigma m(2, 6)$