

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 94303

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2022

Fourth Semester

Electrical and Electronics Engineering

19UEE403 – Principles of Digital Electronics

(Regulations 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- BCD code ranges from CO1- U
(a) 0 to 1 (b) 0 to 9 (c) 0 to 15 (d) 0 to 7
- Identify the even parity code from the following CO1- U
(a) 11001 (b) 1110 (c) 0111 (d) 0110
- What will be the number of selection lines in a 16 to 1 Multiplexer? CO1-U
(a) Type- 0 (b) Type -1 (c) Type -2 (d) Type - 3
- Find the number of the gates required to build a half adder are CO1- U
(a) EX-OR gate and NOR gate (b) EX-OR gate and NOR gate
(c) EX-OR gate and AND gate (d) Four NAND gates
- What is the output of SR flip flop when S=1, R=0 is? CO1-U
(a) 1 (b) 0 (c) No change (d) High impedance
- What is output of D Flipflop when D=1? CO1- U
(a) 1 (b) 0 (c) No Change (d) X
- How many natural states will there be in a 4-bit ripple counter? CO1- U
(a) 4 (b) 8 (c) 16 (d) 32

8. How much storage capacity does each stage in a shift register represent? CO1- U
 (a) One bit (b) two bits (c) four bits (d) eight bits
9. The Verilog HDL code starts with the keyword CO1- U
 (a) always (b) module (c) end module (d) items
10. Which of the following loops are supported by verilog? CO1- U
 (a) if-else loop (b) for loop (c) while loop (d) All the above

PART – B (5 x 2= 10 Marks)

11. Convert the following decimal numbers to the indicated bases CO1- U
 7526.75 to (?)₈ b) 1856.959 to (?)₁₆
12. Define SOP and POS. CO1- U
13. Define a sequential logic circuit. Give an example. CO1- U
14. Define Races CO1- U
15. Explain the purpose of developing HDL code for digital design. CO1- U

PART – C (5 x 16= 80Marks)

16. (a) Convert the following CO1- U (16)
 (147.3)₈ to ()₁₆
 (010010101000)₂ to ()₁₆
 (38.21)₁₀ to ()₂
 (231.3)₁₀to ()₈
- Or
- (b) Explain the types of weighted and non-weighted codes with an example for each type. CO1- U (16)
17. (a) (i) Design a Binary to Gray code converter. CO2- App (8)
 (ii) Design a half adder and implement using logic gates. CO2- App (8)
- Or
- (b) (i) Implement the given function using 8 X 1 MUX $F(A,B,C,D) = \sum m(0, 1,2, 6,7,8,9,10,11,12,15)$ CO2- App (8)
 (ii) Design 3 to 8 decoder using logic gates. CO2- App (8)
18. (a) Design a sequence detector to detect the sequence 101 using JK flip-flops. CO2- App (16)
- Or
- (b) Design synchronous sequential circuit that goes through the count sequence 1,3,4,5 repeatedly. Use T flip-flops for your design. CO2- App (16)

19. (a) An asynchronous sequential circuit has two internal states and one output. The excitation and output function describing the circuit are as follows. $Y_1 = x_1.x_2 + x_1.y_2 + x_2.y_1$, $Y_2 = x_2 + x_1.y_1.y_2 + x_1.y_1$
 $Z = x_1 + x_2$
 (i) Draw the logic diagram of the circuit.
 (ii) Derive the transition table and output map.
 Describe the behavior of the circuit.
 Or
- (b) An asynchronous sequential circuit is described by the following excitation and output equation. $Y = x_1.x_2 + (x_1 + x_2).y$ $Z = Y$
 (i) Draw the logic diagram of the circuit.
 (ii) Derive the transition table and output map.
 Describe the behavior of the circuit.
20. (a) Implement the following function using PLA, $A(x,y,z) = \sum m(1,2,4,6)$ $B(x,y,z) = \sum m(0,1,6,7)$ $C(x,y,z) = \sum m(2,6)$. CO2- App (16)
 Or
- (b) Develop Verilog code to design 8 to 1 multiplexer using dataflow and behavioural modeling. CO2- App (16)

