

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code:U2B05**

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Second Semester

Biomedical Engineering

21UBM205- HUMAN ANATOMY AND PHYSIOLOGY

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)


- Ohms law holds true only for \_\_\_\_\_ circuits CO1- U  
(a) Linear (b) Non-linear (c) Unilateral (d) None of the above
- Three equal resistances of  $3 \Omega$  are connected in star. What is the resistance in one of the arms in an equivalent delta circuit CO2- U  
(a)  $10 \Omega$  (b)  $3 \Omega$  (c)  $9 \Omega$  (d)  $27 \Omega$
- What is the total reactance of a series RLC circuit at resonance? CO2- U  
(a) Equal to  $X_L$  (b) Equal to  $X_C$  (c) Equal to R (d) Zero
- Which amplifier is used in an electronic multimeter? CO4- U  
(a) Wideband amplifier (b) Differential amplifier  
(c) Buffer amplifier (d) Power amplifier
- Fuse protection is used for current ratings up to CO5- U  
(a) 10 A (b) 20 A (c) 50 A (d) 100 A

PART – B (5 x 3= 15 Marks)

- Define ideal voltage source CO1- U
- Define Norton Theorem CO2- U
- What do you understand by resonance? CO3- U
- List the difference between CT and PT CO4- U
- What is the purpose of earthing? CO5- U


PART – C (5 x 16= 80Marks)

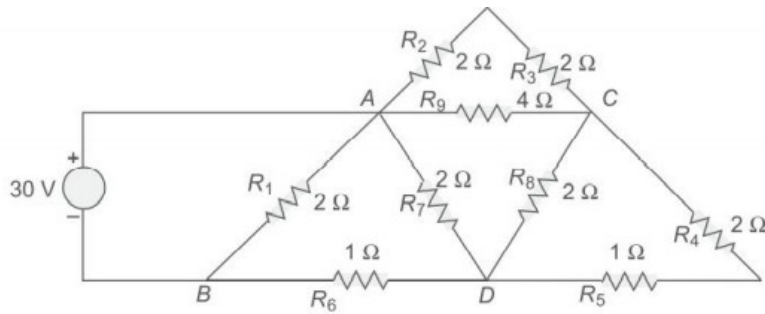11. (a) Determine the current delivered by the source in the circuit shown in Fig CO1-App (16)  
in Fig




Or

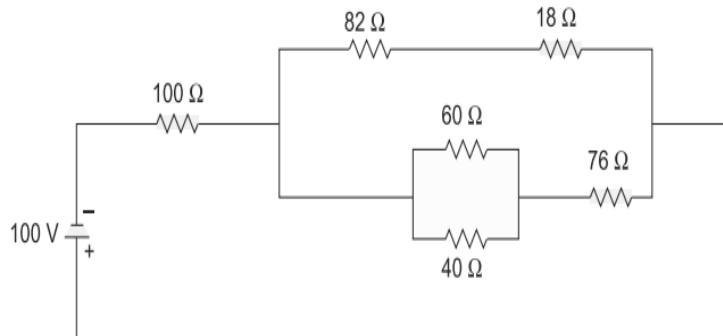- (b) For the circuit shown in Fig., find the total resistance. CO1-App (16)




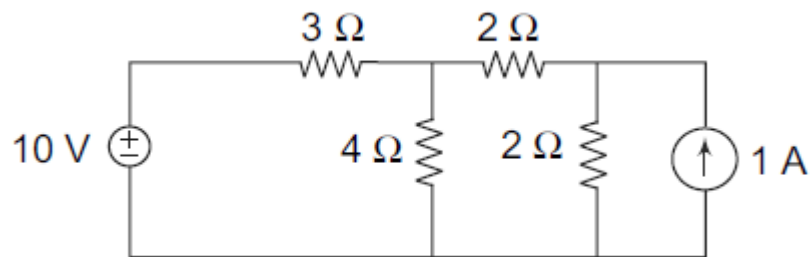12. (a) Calculate the current in the 4 Ω resistor of using the superposition theorem. CO2-App (16)  
theorem.



Or

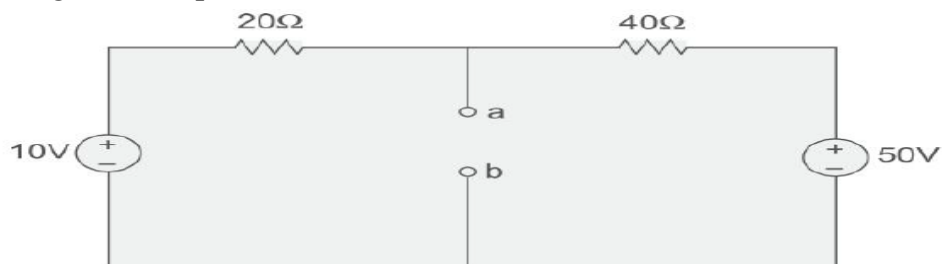
- (b) Find the Thevenin's and Norton's equivalents for the circuit shown in Fig. with respect to terminals ab. CO2-App (16)  
in Fig. with respect to terminals ab.



13. (a) A series RLC circuit has a quality factor of 5 at 50 rad/s. The current flowing through the circuit at resonance is 10 A and the supply voltage is 100 V. The total impedance of the circuit is 20 V. Find the circuit constants

Or

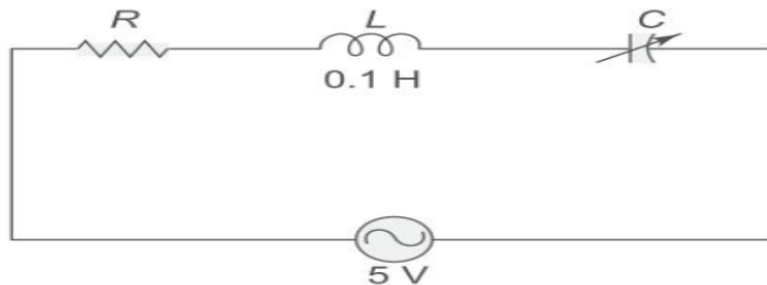- (b) In the circuit shown in Fig. a maximum current of 0.1 A flows through the circuit when the capacitor is at 5  $\mu\text{F}$  with a fixed frequency and a voltage of 5 V. Determine the frequency at which the circuit resonates, the bandwidth, the quality factor Q and the value of resistance at resonant frequency



14. (a) Explain the construction and working principle of PMMC type instrument with necessary diagram

Or

- (b) Elucidate the construction and working principle of an energy meter with necessary circuit arrangement

15. (a) Explain the various methods of electrical wiring system

Or

- (b) What are the basic concepts of household wiring and explain?

