

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code :R3B02**

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Third Semester

Biomedical Engineering

R21UBM302-DIGITAL LOGIC CIRCUITS


(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

PART A - (10 x 2 = 20 Marks)

 1. Implement Boolean expression for EX - OR gate using NAND gates only. CO2-App
2. State De-Morgan's theorem. CO1-U
3. The output of the combinational circuit given below is CO2-App



4. Why carry look ahead adder is faster than ripple carry adder and full adder? CO1-U
5. How many flip-flops are required to build a binary counter that counts from 0 to 7? CO1-U
6. Distinguish between synchronous counter and asynchronous counter. CO1-U
7. Define Hazards and How it can be avoided? CO1-U
8. Classify Asynchronous sequential circuits. CO1-U
9. Why RAMs are called as Volatile? CO1-U
10. How programmable logic devices are classified? CO1-U

PART - B (5 x 16= 80 Marks)

11. (a) Plot the following logical Expression on a 4-variable K - map CO2-App (16)  
 $F=ABCD+AB'C'D'+AB'C+AB$  & realize the SOP using only NAND gates and POS using only NOR gates.  
OR  
(b) Find a minimal sum-of-products for the Boolean expression CO2-App (16)  
 $f(w, x, y, z) = \sum m(1,2,3,7,8,9,10,11,14,15)$  using various methods and justify your answer.

12. (a) (i) Discuss about the design of 4-bit BCD adder with neat diagram and mention how many adders are used in the BCD circuit CO2-App (8)
- (ii) Analyze the principle and design of Parallel binary adder with diagrams. CO2-App (8)
- OR
- (b) (i) Implement the following functions using Multiplexers. CO2-App (8)  
 $F(A,B,C,D) = \sum m(0,1,3,4,8,9,15)$
- (ii) Draw the logic diagram of binary to octal decoder and explain the working in detail. CO2-App (8)
13. (a) (i) Design for a 4-bit ring counter using J-K flip flops and D flip flop and justify your answer. CO3-App (8)
- (ii) Realize D flip-flop using SR flip-flop. CO1-U (8)
- OR
- (b) (i) Design MOD 6 Unit distance counter using JK flip-flop. CO3-App (8)
- (ii) Describe the operation of universal shift register with neat block diagram. CO1-U (8)
14. (a) Design an asynchronous sequential circuit with two input A and B and one output C. Initially both inputs are equal to zero. When A or B becomes 1 the output C becomes 1. When the second input also becomes 1, the output changes to 0. The output stays at 0 until the circuits goes back to the initial state. CO4-App (16)
- OR
- (b) (i) Design a sequence detector that produces an output 1 whenever the sequence 101101 is detected. CO4-App (10)
- (ii) Design a circuit that has no static hazards and implement the Boolean function  $F(A,B,C,D) = \sum (0,2,6,7,8,10,12)$  using AND-OR logic. CO4-App (6)
15. (a) Implementation the following Boolean function using PAL. CO5-App (16)  
 $W(A,B,C,D) = \sum m(0,2,6,7,8,9,12,13)$   
 $X(A,B,C,D) = \sum m(0,2,6,7,8,9,12,13,14)$   
 $Y(A,B,C,D) = \sum m(2,3,8,9,10,12,13)$   
 $Z(A,B,C,D) = \sum m(1,3,4,6,9,12,14)$
- OR
- (b) Design PLA, PAL realizations of a full-adder with inputs A, B, C and outputs Sum and Carry. CO5-App (16)

