

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: R2205

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Second Semester

Computer Science and Engineering

R21UCS205- DIGITAL ELECTRONICS

(Common to Cyber Security Engineering branch)

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

- Hexadecimal Value for 15 is equal to _____ CO1- U
(a) A (b) B (c) F (d) D
- How many AND gates required for 1 to 8 MUX? CO2- AP
(a) 2 (b) 3 (c) 4 (d) 8
- When both inputs of a J-K flip-flop cycle, the output will _____ CO1- U
(a) Be invalid (b) Change (c) Not change (d) Toggle
- In synchronous circuit, the present state is determined by CO1- U
(a) unclocked flip-flops (b) clocked flip-flops (c) flip-flops (d) latches
- For programmable logic functions, which type of PLD should be used? CO1- U
(a) PLA (b) PAL (c) CPLD (d) SLD

PART – B (5 x 3= 15 Marks)

- Define Number system. CO1- U
- Define Encoder. CO1- U
- What are the different types of flip-flop? CO1- U
- Define Asynchronous sequential circuit? CO1- U
- Define address of a memory. CO1- U

PART – C (5 x 16= 80 Marks)

11. (a) Solve the following: CO2- AP (16)
 i) $(1001010.1101001)_2$ to base_{10}
 ii) $(15.32)_{10}$ to base_2
 iii) $(1011DA)_{16}$ to base_{10}
 Or
- (b) Simplify the expression using k-map CO2- AP (16)
 $F(A, B, C, D) = \sum(0, 2, 4, 6, 12, 14, 15, 8, 10)$
12. (a) Design Full Adder and derive expression for Sum and Carry in $C_{in}(X, y)$ with circuit diagram. CO2- AP (16)
 Or
- (b) Design a logic circuit that accepts a 4-bit binary code and converts it to 4-bit Gray code with input (B_3, B_2, B_1, B_0) and output (G_3, G_2, G_1, G_0) . CO2- AP (16)
13. (a) Explain the operation of clocked JK flip-flops with suitable diagrams? CO1- U (16)
 Or
- (b) Explain the following Shift Registers in detail CO1- U (16)
 a) SIPO b) PISO c) PIPO
14. (a) Explain in detail about asynchronous sequential with neat block diagram and also discuss design procedure with its suitable example. CO1- U (16)
 Or
- (b) Explain in detail about Hazards and its types with example? CO1- U (16)
15. (a) Explain in detail about the classification of memories with neat block diagram? CO1- U (16)
 Or
- (b) Explain the Characteristic function of TTL and CMOS circuits in Logic families. CO1- U (16)