

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: U4408

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2024

Fourth Semester

Electronics and Communication Engineering

21UEC408-PRINCIPLES OF LINEAR INTEGRATED CIRCUITS

(Regulations 2021)


Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

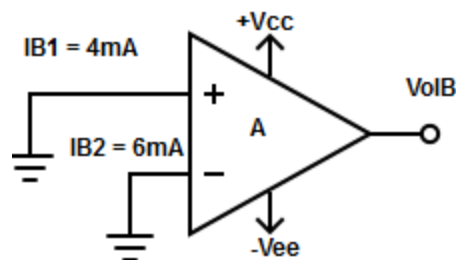1. What is the use of notch and dot in DIP ICs? CO1-U
 - (a) Determine the pin configuration
 - (b) Designed to represent device type
 - (c) Represent property of IC
 - (d) Find the pin number
2. What makes the output voltage equals to zero in practical op-amp? CO1-U
 - (a) Input offset voltage
 - (b) Output offset voltage
 - (c) Offset minimizing voltage
 - (d) Error voltage
3. Find the input bias current for the circuit given below CO3- App



- (a) 10mA
 - (b) 5mA
 - (c) 2mA
 - (d) 6mA
4. At which state the phase-locked loop tracks any change in input frequency? CO1- U
 - (a) Free running state
 - (b) Capture state
 - (c) Phase locked state
 - (d) All of the above

5. How many control lines are present in analog to digital converter in addition to reference voltage? CO1- U
- (a) Three (b) Two (c) One (d) None of the above

PART – B (5 x 3= 15 Marks)

6. Define an Integrated circuit. CO1- U
7. The output of an operational amplifier is 5V peak sine wave whose slew rate is $0.5\text{V}/\mu\text{s}$. Find the maximum allowable frequency of the signal. CO2-App
8. Draw the output waveform of a clipper circuit with input signal amplitude of 5V and reference voltage of +2V. CO3-App
9. In a Monostable Multivibrator using 555 timer, $R=100\text{k}\Omega$ and the time delay is 100ms. Solve for the value of C. CO5-App
10. If the analog signal V_a is +4.129V .Find the equivalent digital number using dual slope ADC. CO6-App

PART – C (5 x 16= 80 Marks)

11. (a) Discuss in detail about the basic planar process in fabrication of ICs. CO1-U (16)
- Or
- (b) Explain in detail about silicon wafer preparation and photolithography. CO1-U (16)
12. (a) (i) Explain the circuit which produce the output with 180° phase shift of the input signal and also produce the output with 0° phase shift of the input signal. CO1-U (16)
- (ii) Illustrate the function of the current source which provides constant current in the load.
- Or
- (b) Explain the DC characteristics of an operational amplifier. CO1-U (16)
13. (a) Design the circuit which is used to produce the integration and differentiation of the input square input signal. CO3- App (16)
- Or
- (b) Design a Schmitt trigger that produces square wave from input sine wave. CO3- App (16)
14. (a) Design an Astable Multivibrator using IC 555 with its frequency of oscillation is 1 KHz. CO4- App (16)

Or

- (b) Determine the change in DC control voltage V_c during lock, if input signal frequency $f_s = 10$ KHz, the free running frequency is 10.66 KHz and the V/F transfer coefficient of VCO is 6600 Hz/V and analyze the same with $f_s = 20$ KHz input signal. CO4- App (16)
15. (a) Design a 3 bit weighted resistor DAC with neat diagram. CO6- App (16)
- Or
- (b) Design an 8 bit the successive approximation ADC with neat diagram. CO6- App (16)

