

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: R2405

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Second Semester

Electronics and Communication Engineering

R21UEC205- ELECTRONIC DEVICES

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5 x 1 = 5 Marks)

- In N-type semiconductor, the current flow is due to the movement of CO1 -U
a) holes b) electrons c) both holes & electrons d) none of above
- In a BJT, if $\beta = 100$, then $\alpha =$ CO2 -App
a) 99 b) 0.99 c) 1.0 (d) 1.01
- The SI Units of the Process trans conductance Parameter is CO1-U
a) V^2/A b) A/V^2 c) V/A d) A/V
- During reverse bias, a small current develops known as _____. CO1-U
(a) Forward current (b) Reverse current
(c) Reverse Saturation Current (d) Leakage Current
- In a BJT, if $\alpha = 0.98$, then $\beta =$ CO1 -U
a) 49 b) 98 c) 47 d) 100

PART – B (5 x 3= 15 Marks)

- How to increase the conductivity of semiconductor? CO3 -App
- Differentiate CE and CB by their input characteristics CO1 -App
- Compare N channel JFET and P channel JFET CO1- U
- Give some applications of photo diodes CO1- U
- Give the condition for biasing arrangement of an NPN transistor to operate in the active region CO1- U

PART – C (5 x 16= 80 Marks)

11. (a) Explain the working of PN junction diode under different bias conditions CO1- U (16)
- Or
- (b) Elaborate the functions of UJT and their characteristics with suitable application. CO1- U (16)
12. (a) Analyze impedance, admittance and gain of transistors to design amplifier with suitable configuration. CO4-An (16)
- Or
- (b) Analyze the current amplification factors of CB, CC and CE configuration and give the relation between α, β and also derive the relation between α, β and Y . CO4-An (16)
13. (a) Explain the construction, working and operating characteristics of N-channel JFET with relevant diagrams. CO1- U (16)
- Or
- (b) Derive the expression for depletion N channel MOSFET with suitable characteristic parameters CO1- U (16)
14. (a) Design a half wave rectifier using PN diode and calculate ripple factor and efficiency CO1- U (16)
- Or
- (b) Compute the V_{dc} , V_{rms} , efficiency and peak factor of bridge rectifier. CO1-U (16)
15. (a) (i) The common base DC current gain of the transistor 0.967.If the emitter current is 10mA.What is the value of base current.
(ii) A transistor has $I_E=10mA, \alpha=0.98$.Determine the value of I_C, I_B CO3-App (16)
- Or
- (b) (i) Determine the value of I_C and I_B for the transistor circuit of $I_E=12mA, \beta=100$ CO3-App (16)
(ii) A current gain of transistor in CE mode is 49.Calculate its common base current gain. Find the base current when the emitter current is 3Ma