

C

Reg. No. :

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

**Question Paper Code: R2425**

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Second Semester

Computer Science and Business Systems

R21UEC225- PRINCIPLES OF ELECTRONICS ENGINEERING

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

- Ripple factor of half wave rectifier is \_\_\_\_\_ CO1-U  
a) 1.414                      b) 1.21                      c) 1.3                      d) 0.48
- The base of transistor is CO1-U  
a) heavily doped    b) moderately doped    c) lightly doped    d) none
- For a FET when will maximum current flows? CO1- U  
(a)  $V_{gs} = 0V$     (b)  $V_{gs} = 0v$  and  $V_{ds} \geq |V_p|$     (c)  $V_{DS} \geq |V_p|$     (d)  $V_p = 0$
- What is the gray code for the binary number: 1011100010? CO2-U  
(a) (0110010011)    (b) (00110010011)    (c) (1110010011)    (d) (0010010011)
- Which of these flip – flops cannot be used to construct a serial shift register? CO2 -U  
(a) D – flip flop    (b) SR flip – flop    (c) T flip – flop    (d) JK flip – flop

PART – B (5 x 3= 15 Marks)

- List the applications of Zener diode. CO1-U
- Give the relation between  $\alpha$  and  $\beta$ . CO1- U
- Define amplification factor in JFET. CO1 -U
- Draw the logical symbol and truth table of 2-input Ex-NOR Gate. CO2-U
- List the types of Shift registers. CO2- U

PART – C (5 x 16= 80 Marks)

11. (a) Draw and explain the energy band diagram for the following CO1-U (16)  
(i) conductors (ii) Insulators (iii) semiconductors  
Or
- (b) Explain the working principle of half wave rectifier with neat sketch. Also, derive the various parameters associated with it. CO1-U (16)
12. (a) Distinguish between the different types of transistor configurations with necessary circuit diagrams. Also, obtain the relation between the current amplification factors  $\alpha$ ,  $\beta$  and  $\gamma$  of a transistor. CO1- U (16)  
Or
- (b) Construct a circuit which is used for amplifier application. Also, draw input and output characteristics for the circuit. Obtain the relation between the current amplification factor of  $\alpha$ ,  $\beta$  and  $\gamma$  of a transistor CO1- U (16)
13. (a) “Field Effect Transistor is a voltage controlled current device”.- CO1- U (16)  
Justify the statement by describing the characteristics of the device involving the impact of various parameters such as pinch-off voltage, source drain voltage and gate source voltage.  
Or
- (b) Discuss your understanding on MOSFET detailing the types, CO1- U (16)  
construction and characteristics.
14. (a) Minimize the given Boolean function using K-map and implement the minimized function using appropriate logic gates. CO4 -App (16)  
 $F(A,B,C,D)= \Sigma m(3,4,5,7,9,13,14,15)$   
Or
- (b) Implement 8 to 1 Multiplexer with appropriate truth table and logic diagram. CO4- App (16)
15. (a) Make use of clocked S-R flip-flop to formulate the excitation table of J-K flip-flop and characteristic equation from its characteristic table. CO4 -App (16)  
Or
- (b) Explain Parallel –in-parallel-out (PIPO) shift register with necessary waveforms. CO4 -App (16)