

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: R3405

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Third Semester

Electronics and Communication Engineering

R21UEC305 – ELECTRONIC CIRCUITS

(Regulation R2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

1. Improper biasing of a transistor circuit leads to ----- CO1-U
 - a) Excessive heat production at collector terminal.
 - b) Distortion in output signal
 - c) Faulty location of load line
 - d) Heavily loading of emitter terminal.
2. The capacitive effects of transistor junction manifest themselves in CO1-U
 - a) Low frequency
 - b) high frequency
 - c) middle frequency
 - d) all the above
3. For a transistor $T_J=160^\circ\text{C}$, $T_A=40^\circ\text{C}$ and $\theta_{J-A}=80^\circ\text{C}$ Calculate the power that the transistor can safely dissipate in free air CO2- App
 - (a) 2.3W
 - (b) 5.8W
 - (c) 4.0W
 - (d) 1.5W
4. When current feedback (negative) is applied to an amplifier, its input impedance CO1-U
 - (a) Is decreased
 - (b) Is increased
 - (c) Remains the same
 - (d) None of the above
5. For a phase shift oscillator the gain of the amplifier stage must be greater than CO1-U
 - (a) 19
 - (b) 29
 - (c) 30
 - (d) 1

PART – B (5 x 3= 15Marks)

6. Define thermal runaway. CO1-U
7. State Miller's theorem CO1-U

- | | | |
|-----|---|-------|
| 8. | What is crossover distortion? How it can be eliminated | CO1-U |
| 9. | Define the Nyquist criterion of stability. | CO1-U |
| 10. | Write down the advantages of RC phase shift oscillator. | CO1-U |

PART – C (5 x 16= 80 Marks)

- | | | | |
|-----|--|----------|------|
| 11. | (a) Derive the expression of stability factor for a bipolar junction transistor with a common emitter configuration by applying your understanding of potential divider bias. | CO2-App | (16) |
| | Or | | |
| | (b) Derive the necessary expressions and analyze Voltage gain (A_v), Current Gain(A_i), Input Impedance(Z_i), output admittance(Y_o) from small signal model of BJT using h-parameters for Common emitter configurations of BJT. | CO2-App | (16) |
| 12. | (a) Analysis the BJT circuit for LF amplifier coupling capacitors C_1 and C_2 are used to block DC components and allow AC signals to pass. The emitter bypass capacitor C_{EC_ECE} improves the amplifier's AC gain. | CO4-Ana | (16) |
| | Or | | |
| | (b) Analysis the BJT circuit for HF amplifier coupling capacitors C_1 and C_2 are used to block DC components and allow AC signals to pass. The emitter bypass capacitor C_{EC_ECE} improves the amplifier's AC gain. | CO4-Ana | (16) |
| 13. | (a) Prove that the class B power amplifier provides the efficiency of 78.5% by calculating its input and output power. Also explain its operation | CO1-U | (16) |
| | Or | | |
| | (b) Explain the operation of class A transformer coupled power amplifier circuit using power transistor and calculate its maximum efficiency. | CO1-U | (16) |
| 14. | (a) Design a Voltage- series, feedback amplifier for deriving voltage gain, input resistance and output resistance. Assume necessary data | CO2- App | (16) |
| | Or | | |
| | (b) Design a feedback amplifiers to derive the input and output resistance for shunt-series feedback connection. Assume necessary data | CO2- App | (16) |

15. (a) Explain Colpitts oscillator and derive the equation for oscillation? CO1-U (16)
- Or
- (b) Discuss about Wein bridge oscillator and derive its frequency of oscillation. CO1-U (16)

