

**A**

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: R2305**

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Second Semester

Electrical and Electronics Engineering

R21UEE205- ELECTRIC CIRCUIT ANALYSIS

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (10 x 1 = 10 Marks)

- Which among the following is true about ohm's law? CO1-U  
(a)  $I \propto V$                       (b)  $I = V/R$                       (c)  $V = IR$                       (d) All of these
- Two bulbs B1 100 W, 200 V and B2 40 W, 200 V are connected in series across 200 V battery, the total circuit resistance will be CO1-U  
(a) 1000  $\Omega$                       (b) 400  $\Omega$                       (c) 1400  $\Omega$                       (d) 135  $\Omega$
- An alternating voltage is given by  $V = V_m \sin 157t$ . The frequency of the alternating voltage is \_\_\_\_\_ CO1-U  
(a) 50Hz                      (b) 25Hz                      (c) 100Hz                      (d) 75Hz
- The power factor of an AC circuit is equal to CO1-U  
(a) Cosine of the phase angle                      (b) Sine of the phase angle  
(c) Unity for a resistive circuit                      (d) Unity for a reactive circuit
- When the power transferred to the load is maximum, the efficiency of power transfer is CO1-U  
(a) 25%.                      (b) 100%.                      (c) 75%.                      (d) 50%
- For high efficiency of transfer of power, internal resistance of the source should be CO1-U  
(a) equal to the load resistance                      (b) less than the load resistance  
(c) more than the load resistance                      (d) none of the above


7. The power factor is unity for the \_\_\_\_\_ resonant circuit CO1-U  
 (a) Series (b) parallel (c) both a & b (d) none
8. The power factor is unity for the \_\_\_\_\_ resonant circuit. CO1-U  
 (a) Series (b) parallel (c) both a & b (d) none
9. If the resistance in parallel with a parallel resonant circuit is reduced, the bandwidth CO1-U  
 (a) Disappears (b) Becomes sharper  
 (c) Increases (d) Decreases
10. If the roots of an equation are complex conjugate, then the response will be? CO1-U  
 (a) over damped (b) critically damped (c) damped (d) under damped

PART – B (5 x 2= 10 Marks)

11. In a circuit three resistors  $R_1 \Omega$ ,  $R_2 \Omega$  and  $R_3 \Omega$  are connected in series. What is the total resistance CO1 U
12. Define form factor CO1 U
13. Draw the Norton's equivalent circuit CO1 U
14. Compare series and parallel resonance CO1 U
15. What is damping ratio?. CO1 U


PART – C (5 x 16= 80 Marks)

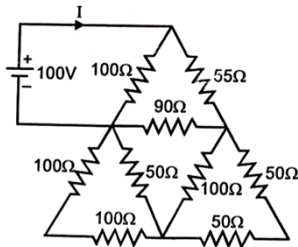16. (a) Briefly explain about the connections of resistance in the circuit CO2-App (16)  
 Solve the total current taken from the source.



Or

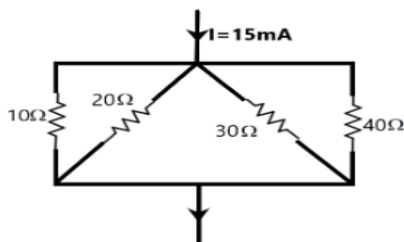
- (b) Using the current division rule, find the current in each branch of the circuit shown in the figure. CO2-App (16)



17. (a) A resistor of  $6\ \Omega$  and an inductor of  $25.5\text{mH}$  are connected in series across  $220\text{V}$ ,  $50\text{Hz}$  supply. Find (1) Inductive reactance (2) Impedance (3) Current (4) Phase angle (5) Power factor (6) Power (7) Voltage across the resistor and(8) Voltage across inductor CO2- Ana (16)


Or

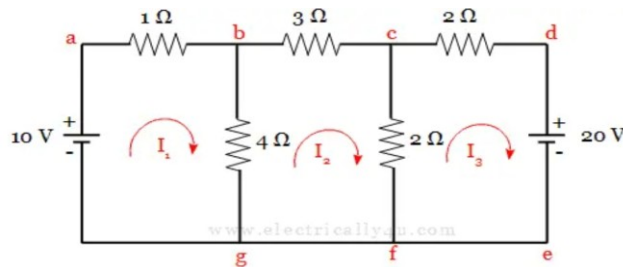- (b) With a neat circuit and phasor diagram explain the three phase power measurement by two wattmeter method. CO2- App (16)
18. (a) Find the current through  $10\ \Omega$  load resistor using mesh current analysis CO2- App (16)



Or

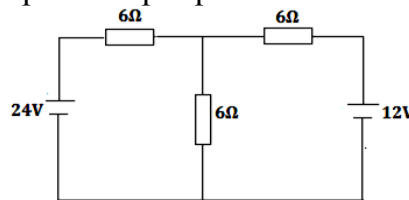- (b) Find the current through load resistor ( $6\ \Omega$ ) in the following circuit by the principle of super position theorem CO2- App (16)



19. (a) Consider an RLC circuit consisting of a resistor (R), inductor (L), and capacitor (C) connected in series. The values of R, L, and C are given as follows:  $R = 5\ \Omega$ ,  $L = 40\text{mH}$ , and  $C = 1\ \mu\text{F}$ . Answer the following questions based on this circuit: CO4-Ana (16)
- (a) Calculate the resonant frequency ( $f_r$ ) of the circuit.
  - (b) Determine the Q-factor (Quality factor) of the circuit.
  - (c) Calculate the bandwidth of the circuit.
  - (d) Half Power frequencies.


Or

- (b) Consider a series RLC circuit consisting of a resistor ( $R = 10 \Omega$ ), an inductor ( $L = 30 \text{ mH}$ ), and a capacitor ( $C = 1 \mu\text{F}$ ), and is supplied from a 10V variable frequency source. Analyze the circuit using the concept of resonance and answer the following questions:

Find the frequency for which the voltage developed across the capacitor is a maximum and calculate the magnitude of this voltage.

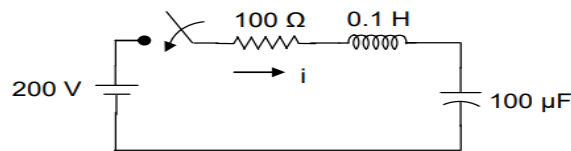20. (a) For the RLC circuit shown, find the expression for the transient current

When the switch is closed at time  $t = 0$ . Assume initially relaxed circuit conditions



Or

- (b) Consider a series RC circuit consisting of a resistor ( $R = 1 \text{ k}\Omega$ ) and a capacitor ( $C = 1 \mu\text{F}$ ). The circuit is initially at rest, and a voltage step of 10 V is applied at  $t = 0$ . Analyze the circuit's transient response and answer the following questions:

(a) Calculate the time constant ( $\tau$ ) of the circuit.

(b) Determine the natural response of the circuit and explain its behavior over time.

(c) Calculate the initial capacitor voltage ( $V_c(0)$ ) in the circuit when the voltage step is applied.

(d) Determine the complete solution for the capacitor voltage ( $V_c(t)$ ) in the circuit as a function of time.