

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: R2804

B.E./B.Tech. DEGREE EXAMINATION, NOV 2024

Second Semester

Information technology

R21UIT204 - DIGITAL PRINCIPLES & SYSTEM DESIGN

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Find 2's complement of $(11000100)_2$ CO2-App
a) $(00111100)_2$ b) $(111111)_2$ c) $(1100010)_2$ d) $(11110101)_2$
- What is the output of that $A + \bar{A}B =$ CO2-App
(a) $A+B$ (b) $B+A$ (c) $A+A$ (d) $A+B$
- The result obtained on binary multiplication of $1010 * 1100$ is _____ CO2-App
(a) 1111000 (b) 1111001 (c) 1111000 (d) 1111001
- The Simplified expression of full subtractor Borrow is _____ CO1-U
(a) $B_{out} = \bar{A}B_{in} + \bar{A}B + BB_{in}$ (b) $B_{out} = BA_{in} + BB + BA_{in}$
(c) $B_{out} = AB_{in} + BA + AA_{in}$ (d) $AB_{in} + BB_{in} + BB_{in}$
- If the number of n selected input lines is equal to 2^m then it requires _____ selected lines CO1-U
(a) n (b) m (c) 2 (d) 2n
- For re programmability, PLDs use _____ CO1-U
(a) PROM (b) EPROM (a) PROM (d) De Multiplexer
- The functional difference between SR flip-flop and JK flip-flop is that CO1-U
(a) JK flip-flop is faster than SR flip-flop (b) JK flip-flop has a feedback path
(c) JK flip-flop accepts both inputs 1 (d) JK flip-flop does not require external clock

8. A counter circuit is usually constructed of _____ CO1-U
 (a) A number of latches connected in cascade form
 (b) A number of NAND gates connected in cascade form
 (c) A number of flip-flops connected in cascade
 (d) A number of NOR gates connected in cascade form
9. A condition occurs when an asynchronous sequential circuit changes two or more binary states variable is _____. CO1-U
 (a) deadlock condition (b) Running condition (c) Race condition (d) None
10. The race in which stable state depends on order is called CO1-U
 (a) critical race (b) identical race (c) non critical race (d) defined race

PART – B (5 x 2= 10Marks)

11. Identify the 2's complement of the following: CO2-App
 (i) 1111111
 (i) 101010
12. Derive the K-map and draw the logic diagram of full-adder CO2-App
13. Draw the truth table and circuit diagram of 4 to 2 encoder. CO2-App
14. Construct the Excitation table for J-K Flip flop CO2-App
15. Outline on Hazards and its effect on circuit CO2-App

PART – C (5 x 16= 80Marks)

16. (a) Minimize the expression using QuineMccluskey method: CO2-App (16)

$$Y = \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + AB\bar{C}\bar{D} + AB\bar{C}D + A\bar{B}\bar{C}D + A\bar{B}C\bar{D}$$

 Or
- (b) Simplify the following Boolean Expression: CO2-App (16)
- i) $Y = AB + A(B + C) + B(B + C)$ (4)
- ii) $Y = \overline{AB}(\bar{A} + B)(\bar{B} + B)$ (4)
- iii) $\overline{Y} = \overline{A\bar{C} + \bar{B}\bar{C} + B\bar{C} + ABC}$ (4)
- iv) $\overline{Y} = A + \bar{A}B + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}D$ (4)
17. (a) Derive the truth table for full adder and simplify the K-map for its outputs. Draw its block schematic and logic diagram of sum of product (SOP) implementation of full adder. CO2-App (16)
- Or
- (b) Design a logic circuit to convert BCD to gray code. CO2-App (16)

18. (a) Realize $F(w,x,y,z)=\sum(1,4,6,7,8,9,10,11)$ using 4 to 1 MUX. CO2-App (16)
 Or
 (b) Design a switching circuit that converts a 4 bit binary code into a 4 bit Gray code using ROM array CO2-App (16)
19. (a) Construct a S-R Flip-Flop with 2-bit input values 00,01,10 & 11 and reclaim its states necessary logic diagram CO2-App (16)
 Or
 (b) Design divide by 6 counter using T-flip-flops. Write state table and reduce the expression using K-map CO2-App (16)
20. (a) Design an asynchronous sequential circuit with two inputs x_1 and x_2 and one output Z . Initially both inputs are equal to zero. When x_1 or x_2 becomes 1 the output Z becomes 1. When the second input also becomes 1 the output changes to 0. The output stays at 0 until the circuit goes back to the initial state. CO2-App (16)
 Or
 (b) Give hazard-free realization for the following Boolean function CO2-App (16)
 $F(A,B,C,D) = \sum (0,2,4,5,8,10,14)$
 $f(A,B,C,D) = \pi (3,4,7,8,9,12,15)$

