

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code:U5406

M.E. DEGREE EXAMINATION, NOV 2024

Professional Elective

Power Electronics and Drives

21PPE506 - MODERN RECTIFIERS AND RESONANT CONVERTERS

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART - A (5 x 20 = 100 Marks)

1. (a) Design the capacitor for minimize the THD in rectifiers CO1-U (20)
Or
(b) Design the rectifier with large capacitor and discuss the behavior in detail. CO1-U (20)
2. (a) Construct the Boost rectifier and derive the expression for controller duty cycle. CO2-U (20)
Or
(b) Construct the Hysteresis control & non linear control methods of rectifiers. CO2-U (20)
3. (a) Analyze the Zero current Switching and Zero Voltage Switching? CO3-App (20)
Or
(b) Analyze the Quasi resonant Boost Converter? CO3-App (20)
4. (a) Derive the State Space Averaged model for an ideal Buck Converter and analyze the performance. CO4-App (20)
Or
(b) Derive the State Space Averaged model for an ideal Boost Converter and analyze the performance. CO4-App (20)
5. (a) Explain about Voltage mode PWM Scheme and Current mode PWM Scheme. CO5-Ana (20)
Or
(b) Explain in detail about Optimal Controller for the source current shaping of PWM rectifiers. CO5-Ana (20)

