

**A**

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code:R2306**

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2025

First Semester

Electrical and Electronics Engineering

R21UEE206 – PRINCIPLES OF ELECTRONICS ENGINEERING

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. The movement of free electrons in a semiconductor due to an applied electric field is called: CO1-U  
(a) Diffusion                      (b) Drift                      (c) Recombination      (d) Ionization
2. The potential barrier for Silicon P-N junction at room temperature is approximately: CO1-U  
(a) 0.7V                      (b) 0.3V                      (c) 1.1V                      (d) 0.1V
3. The relationship between  $\alpha$  and  $\beta$  is given by: CO1-U  
(a)  $\beta = \alpha/(1-\alpha)$                       (b)  $\alpha = \beta/(1+\beta)$                       (c)  $\beta = \alpha/(1+\alpha)$                       (d)  $\alpha = \beta/(1-\beta)$
4. The most commonly used transistor configuration for amplification is: CO1-U  
(a) Common Base                      (b) Common Emitter  
(c) Common Collector                      (d) All of the above
5. In a Depletion-type MOSFET, the channel is: CO1-U  
(a) Physically constructed      (b) Induced by gate      (c) Not present                      (d) Both a and b
6. A JFET is a: CO1-U  
(a) Voltage-controlled device                      (b) Current-controlled device  
(c) Pressure-controlled device                      (d) Temperature-controlled device
7. The purpose of a bypass capacitor in a CE amplifier is to: CO1-U  
(a) Block DC                      (b) Increase gain  
(c) Stabilize bias                      (d) Bypass AC component of emitter current



19. (a) Explain the operation of a small-signal CE amplifier using the hybrid model with a neat circuit diagram **CO1-U (16)**  
or  
(b) With neat sketches, explain the concept and operation of a differential amplifier. **CO1-U (16)**
20. (a) Analyze the frequency stability and amplitude control mechanisms in a Wien Bridge oscillator circuit, and evaluate how component variations affect the oscillator's performance. **CO4-Ana (16)**  
or  
(b) Analyze a crystal oscillator circuit to interpret how its piezoelectric properties determine oscillation, and evaluate the benefits of using it over RC or LC oscillators. **CO4-Ana (16)**

