

**A**

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: R3303**

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2025

Third Semester

Electrical and Electronics Engineering

R21UEE303 – PRINCIPLES OF DIGITAL ELECTRONICS

(Regulations R2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- BCD code ranges from CO1- U  
(a) 0 to 1                      (b) 0 to 9                      (c) 0 to 15                      (d) 0 to 7
- MOS transistor is CO1- U  
(a) voltage controlled voltage device                      (b) current controlled voltage device  
(c) voltage controlled current device                      (d) current controlled current device
- Find the number of the gates required to build a half adder are CO1- U  
(a) EX-OR gate and NOR gate                      (b) EX-OR gate and OR gate  
(c) EX-OR gate and AND gate                      (d) Four NAND gates
- Find the number of outputs for 4 input decoder circuit CO1- U  
(a) 2                      (b) 16                      (c) 4                      (d) 5
- Find the output of D Flip-flop when D=1. CO1- U  
(a) 1                      (b) 0                      (c) No change                      (d) X
- Explain the toggle state in JK Flip-Flop CO1- U  
(a) Set Q = 1 and Q = 0                      (b) Set Q = 0 and Q = 1  
(c) Change the output to the opposite state                      (d) No change in output
- Internal propagation delay of asynchronous counter is removed by CO1- U  
(a) Ripple counter                      (b) Ring counter                      (c) Modulus counter                      (d) Synchronous counter

8. How much storage capacity does each stage in a shift register represent? CO1- U  
 (a) One bit (b) two bits (c) four bits (d) eight bits
9. Verilog HDL is a case-sensitive language. All keywords are in CO1-U  
 (a) lowercase (b) uppercase  
 (c) either lower or uppercase (d) bold letters
10. The keyword @posedge means CO1- U  
 (a) Transition from 0 to 1, x or z (b) Transition from x to 1  
 (c) Transition from z to 1,x (d) All the above

PART – B (5 x 2= 10 Marks)

11. Explain De Morgan's theorem. CO1- U
12. Draw the logic diagram of EX-OR gate using NAND gates. CO1- U
13. Draw the logic diagram of clocked SR flip-flop. Draw the truth table of RS flip flop. CO1- U
14. Implement the following Boolean function using ROM (PROM) CO3- App  
 $F_1 = \sum m(1,2,3); \quad F_2 = \sum m(0,1,3)$
15. Develop Verilog Code to design half adder using gate level modeling. CO3- App

PART – C (5 x 16= 80 Marks)

16. (a) (i) A 12 bit Hamming code word containing 8 bits of data and 4 parity bits is read from memory. What was the original 8 bit data word that was written in to memory if the 12 bit word read out is as A) 101110010100 B)111111110100 CO1- U (10)  
 (ii) Convert the following decimal number to hexadecimal, Octal and Binary. (A)  $(1259)_{10}$  (B)  $(5768)_{10}$  CO1- U (06)  
 Or
- (b) (i) Compare TTL, DTL, RTL and ECL CO1- U (8)  
 (ii) Draw the CMOS logic circuit for NOR gate. CO1- U (8)
17. (a) (i) Simplify the following function using K-Map. CO2- App (10)  
 $F(A,B,C,D) = \sum m(0,1,2,3,4,6,8,9,10,12,14,15)$ .  
 (ii) Design a half subtractor and implement using logic gates. CO2- App (06)  
 Or
- (b) (i) Simplify the following function using K - Map and implement using gates.  $F(P,Q,R,S) = \sum m(0,1,2,4,7,10,11,12)$  CO2- App (10)  
 (ii) Design a full adder and implement using logic gates. CO2- App (06)

18. (a) A sequential circuit has two JK Flip-Flops A and B, one input (x) CO4- Ana (16) and one output (y). the Flip-Flop input functions are,


$$J_A = B + x \quad J_B = A' + x'$$

$$K_A = 1, K_B = 1$$

and the circuit output function,  $Y = x A' B$ . Analyze the synchronous Mealy machine and obtain its state diagram.

Or

 - (b) Analyze the synchronous Mealy machine and obtain its state CO4- Ana (16) diagram.



19. (a) Design a logic circuit for the following Boolean expression using CO3- App (16) PROM.

$$f_1(x, y, z) = \sum m(0,1,2,5,7)$$

$$f_2(x, y, z) = \sum m(1,2,4,6)$$

Or

- (b) Develop a PLA circuit to implement the logic function CO3- App (16)  $A'BC + AB'C + AC'$  and  $A'B'C' + BC$

20. (a) Develop Verilog code to design 8 to 1 multiplexer using dataflow CO3- App (16) and behavioral modeling.

Or

- (b) Write Verilog code to design 3 to 8 decoder using gate level and CO3- App (16) behavioral modeling.

