

Reg. No. : 

--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: U5506**

M.E. DEGREE EXAMINATION, NOV/DEC 2025

Professional Elective

Power Electronics and Drives

21PPE506 - MODERN RECTIFIERS AND RESONANT CONVERTERS

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART - A (5 x 20 = 100 Marks)

- 1. (a) Discuss the operation of a single phase full wave controlled rectifier feeding RL load. What is the effect of adding a freewheeling diode on the performance of the converter? CO1 U (20)  
Or  
(b) Explain the Single phase full wave rectifier-Continuous Conduction Mode with necessary circuit diagram and waveforms. CO1 U (20)
  
- 2. (a) Analyze the Properties of Ideal rectifiers. CO2-Ana (20)  
Or  
(b) Compare the properties of Ideal and Non ideal rectifiers with neat diagram. CO2-Ana (20)
  
- 3. (a) (i) Analyze the operation of zero current switching Quasi-resonant boost converter with neat circuit and waveforms. CO2-Ana (10)  
(ii) Compare ZVS and ZCS topologies. CO2-Ana (10)  
Or  
(b) Analyze the operation of quasi resonant ZVS Boost converter and deduce the expression for dc gain. CO3-Ana (20)
  
- 4. (a) Describe in detail about state space averaged model for an ideal buck converter. CO4-U (20)  
Or

- (b) Write short notes on CO4-U (20)  
    (i) Review of linear system analysis  
    (ii) State space averaging
5. (a) Define Pulse Width Modulation? Explain in detail about CO5- App (20)  
voltage mode PWM scheme with necessary diagram.
- Or
- (b) Describe in detail about design of variable structure controller CO5-App (20)  
for the source current shaping of PWM rectifiers.