

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: U2B05**

B.E./B.Tech. DEGREE EXAMINATION, NOV 2023

Second Semester

Biomedical Engineering

21UBM205- Electrical Circuits and Measurements

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (5x 1 = 5 Marks)

1. The duality property is CO1- R  
(a) competitive      (b) mutual      (c) associative      (d) linear
2. Three equal resistances of  $3 \Omega$  are connected in star. What is the resistance in one of the arms in an equivalent delta circuit CO2- R  
(a)  $10 \Omega$       (b)  $3 \Omega$       (c)  $9 \Omega$       (d)  $27 \Omega$
3. What is the total reactance of a series RLC circuit at resonance? CO2- R  
(a) Equal to  $X_L$       (b) Equal to  $X_C$       (c) Equal to R      (d) Zero
4. Which amplifier is used in an electronic multimeter ? CO4- R  
(a) Wideband amplifier      (b) Differential amplifier  
(c) Buffer amplifier      (d) Power amplifier
5. Fuse protection is used for current ratings up to CO5- R  
(a) 10 A      (b) 20 A      (c) 50 A      (d) 100 A

PART – B (5 x 3= 15 Marks)

6. Explain the source-transformation technique CO1- U
7. Define reciprocity theorem? CO2- U
8. What do you understand by resonance? CO3- U
9. List the difference between CT and PT CO4- U


10. What is the purpose of earthing ?

CO5- U

PART – C (5 x 16= 80Marks)

11. (a) Find the voltage between A and B of the circuit shown in Fig. by mesh analysis.


CO1-App (16)

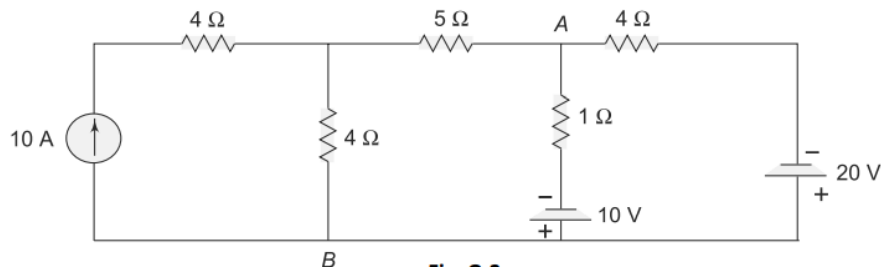

Or


(b) For the circuit shown in Fig., find the total resistance.

CO1-App (16)

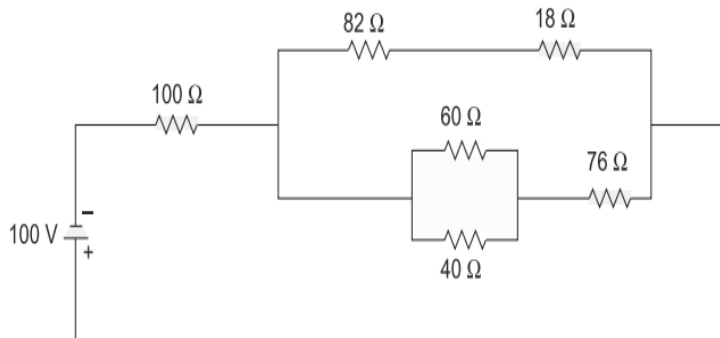


12. (a) Find the current through various branches of the circuit shown in Fig by employing the superposition theorem.

CO2-App (16)

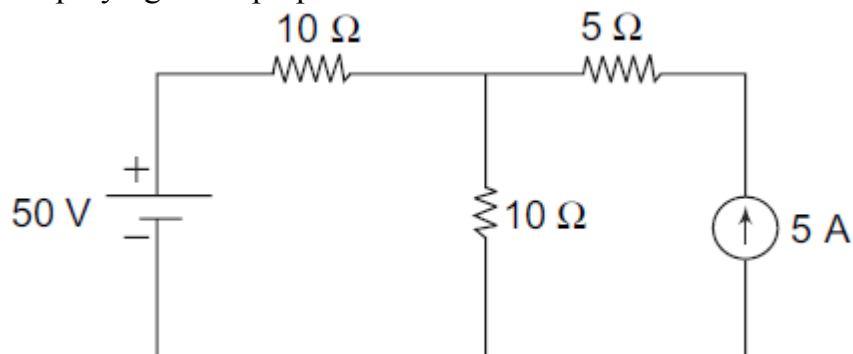

Or

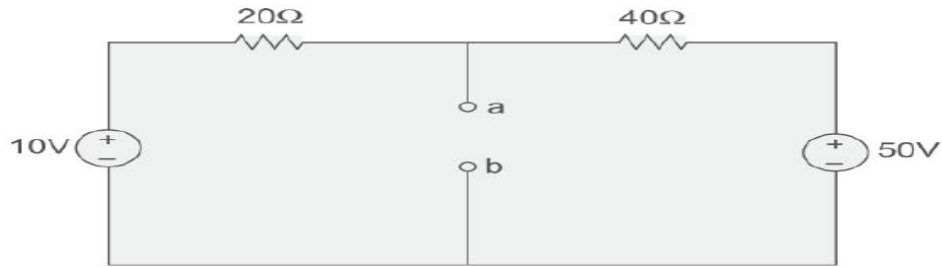
- (b) Find the Thevenin's and Norton's equivalents for the circuit shown in Fig. with respect to terminals ab. CO2-App (16)



13. (a) A series RLC circuit consists of a 50 V resistance, 0.2 H inductance, and 10  $\mu$ F capacitor with an applied voltage of 20 V. Determine the resonant frequency. Find the Q-factor of the circuit. Compute the lower and upper frequency limits and also find the bandwidth of the circuit. CO3-App (16)

Or

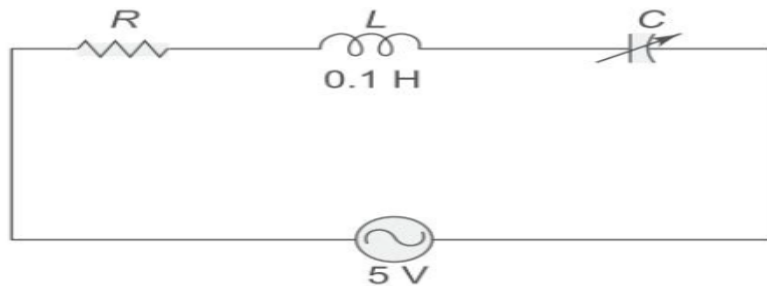- (b) In the circuit shown in Fig. a maximum current of 0.1 A flows through the circuit when the capacitor is at 5  $\mu$ F with a fixed frequency and a voltage of 5 V. Determine the frequency at which the circuit resonates, the bandwidth, the quality factor Q and the value of resistance at resonant frequency CO3-App (16)



14. (a) Draw and explain the working principle of attraction type, repulsion type moving iron instrument CO4-U (16)

Or

- (b) Elucidate the construction and working principle of an energy meter with necessary circuit arrangement CO4-U (16)

15. (a) Explain the different cable and wire types with its application CO5-U (16)

Or

- (b) What are the basic concepts of household wiring and explain? CO5-U (16)

