

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: U3B06

B.E./B.Tech. DEGREE EXAMINATION, NOV 2023

Third Semester

Biomedical Engineering

21UBM306 - DIGITAL LOGIC CIRCUITS

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (10x 2 = 20 Marks)

1. Implement Boolean expression for EX - OR gate using NOR gates only. CO1-App
2. Simplify $(A'+B)(A+B)$ CO1-App
3. Why carry look ahead adder is faster than ripple carry adder and full adder? CO1-App
4. Implement a logic diagram for the device which changes from serial data to parallel data. CO1-App
5. Analyze the differences between Latch and Flip-Flop. CO2-U
6. Mention the steps for the design of asynchronous sequential circuit CO2-U
7. Define dynamic hazard. When do they occur? CO3-U
8. How to differentiate fundamental mode from pulsed mode asynchronous sequential circuit. CO3-U
9. Why RAMs are called as Volatile? CO4-U
10. Differentiate static and dynamic RAM. CO4-U

PART – B (5 x 16= 80 Marks)

11. (a) Find the minimal sum of products for the Boolean expression $F = (A, B, C, D) = \sum (0,2,3,6,7,8,10,11,12,15)$ using Tabulation Method. CO1-App (16)

Or

- (b) Plot the following logical Expression on a 4-variable K – map CO1-App (16)
 $F=ABCD+AB'C'D'+AB'C+AB$ & realize the SOP using only NAND gates and POS using only NOR gates
12. (a) Implement the following Boolean function using an 8:1 multiplexer considering D as the input and A,B,C as selection lines CO2-App (16)
 $F(A, B, C, D) = AB'+BD+B'CD'$
 Or
- (b) Write a brief note on the following combinational circuits: CO2-App (16)
 (i) Full adder (ii) Full subtractor
13. (a) Summarize 4-bit SISO SIPO, PIPO and PISO shift register and draw its waveforms. CO3-App (16)
 Or
- (b) Design for a 4 bit ring counter using J-K flip flops and D flip flop and justify your answer CO3-App (16)
14. (a) Design an asynchronous sequential circuit with two input X and Y and one output Z. The output $Z=1$ if X1 changes from 0 to 1. $Z=0$ if X2 changes from 0 to 1, and $Z=0$ otherwise. CO3-App (16)
 Or
- (b) Design a circuit that has no static hazards and implement the Boolean function $F(A,B,C,D) = \Sigma (0,2,6,7,8,10,12)$ using AND-OR logic. CO3-App (16)
15. (a) Analyze the combinational circuit given below, using PLA CO4-Ana (16)
 $F1(A,B,C) = \Sigma (0,1,2,4)$; $F2(A,B,C) = \Sigma (0,5,6,7)$
 Or
- (b) Implementation the following Boolean function using PAL CO4-Ana (16)
 $W(A,B,C,D)=\Sigma m(0,2,6,7,8,9,12,13)$
 $X(A,B,C,D)=\Sigma m(0,2,6,7,8,9,12,13,14)$
 $Y(A,B,C,D)=\Sigma m(2,3,8,9,10,12,13)$
 $Z(A,B,C,D)=\Sigma m(1,3,4,6,9,12,14)$