

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: U4404**

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2023

Fourth Semester

Electronics and Communication Engineering

21UEC404-LINEAR INTEGRATED CIRCUITS

(Regulations 2021)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

1. A completely compensated inverting amplifier is nulled at room temperature 25°C, determine the temperature at which the total output offset voltage will be zero? CO2-App  
(a) 50°C                      (b) 25°C                      (c) 75°C                      (d) 125°C.
2. Find the gain of the voltage to current converter with grounded load? CO2-App  
(a) 2                              (b) 1                              (c) ∞                              (d) 0
3. In a D-A converter with binary weighted resistor, a desired step size can be obtained by CO1-U  
(a) Selecting proper value of  $V_{FS}$                       (b) Selecting proper value of R  
(c) Selecting proper value of  $R_F$                       (d) All of the mentioned
4. The output of a particular Op-amp increases 8V in 12μs. The slew rate is ..... CO2-App  
(a) 90 v/μs                      (b) 0.67 v/μs                      (c) 1.5 v/μs                      (d) 2.5 v/μs
5. The smallest resistor in a 12 bit weighted resistor DAC is 2.5kΩ, what will be the largest resistor value? CO1-U  
(a) 40.96MΩ                      (b) 10.24MΩ                      (c) 61.44 MΩ                      (d) 18.43MΩ


PART – B (5 x 3= 15Marks)

6. Why an open loop op-amp configuration is not used in linear applications? CO2- App
7. Design an amplifier with a gain of +5. CO1-U

8. Draw an adder circuits using operational amplifier to get the output expression  $V_o = 10V_1 + V_2 + 5V_3$ . CO2-App
9. Why an integrator cannot be made using low pass RC circuit? CO1-U
10. What is the output of a 6 bit ladder D/A converter when it has an input of 101001. For 1 = 10 V and 0 = 0V. CO3-App


PART – C (5 x 16= 80Marks)

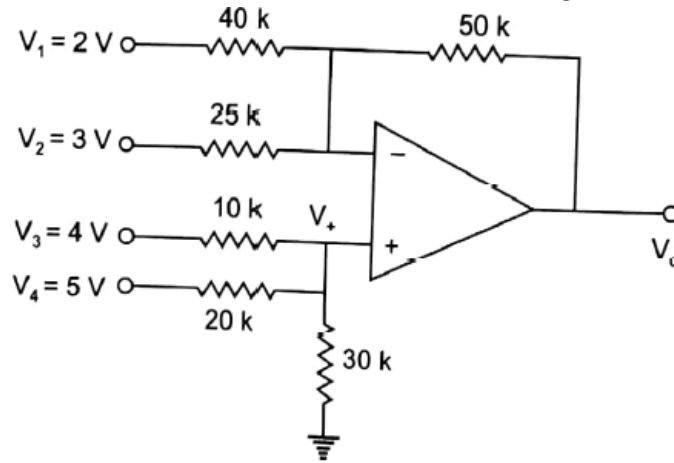11. (a) Explain the DC characteristics of operational amplifier. CO1-U (16)
- Or
- (b) Explain the characteristics of Op – amp when the continuous input is applied at its input terminals. CO1-U (16)
12. (a) Find  $V_o$  for adder- subtractor as shown in fig. CO2-App (16)



Or

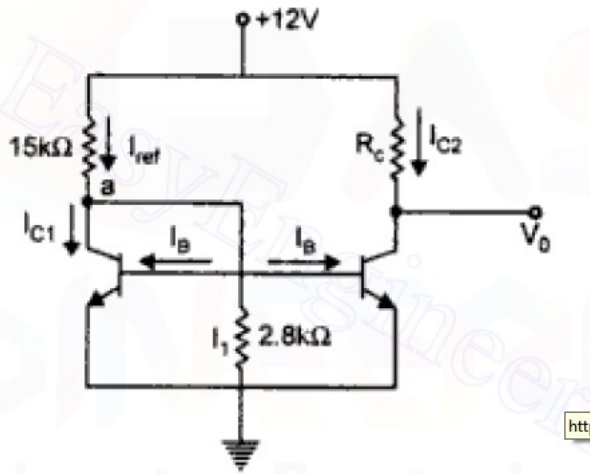- (b) For the circuit shown in Fig. CO2-App (16)
- i) Determine  $I_{c1}$  and  $I_{c2}$
  - ii) Find  $R_c$  so that  $V_o = 6V$ . Assume  $\beta = 200$ .



13. (a) Design an Amplifier circuit to measure the low input signal which is used in industrial and consumer applications. CO2-App (16)
- Or
- (b) Design the circuits which produce triangular and spike wave output for square input signal. CO2-App (16)
14. (a) Design a Monostable operation using 555 timer with its frequency of oscillation is 1 KHz. CO1- U (16)
- Or
- (b) Design a current source using IC 7805 voltage regulator. CO1-U (16)
15. (a) Design a 3 bit weighted resistor DAC with neat diagram. CO3- App (16)
- Or
- (b) Design a 3 bit output Flash type ADC with neat diagram. CO3-App (16)

