

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 96302

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2023

Sixth Semester

Electrical and Electronics Engineering

19UEE602 – POWER SYSTEM ANALYSIS

(Regulations 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. Base impedance per phase is given by.... CO1- R
(a) KV_b / MVA_b (b) KV_b^2 / MVA_b (c) MVA_b / KV_b^2 (d) MVA_b^2 / KV_b
2. In an n-bus power system, considering n nodes network, the size of the Y_{bus} is.... CO1- U
(a) $(n-1) \times (n-1)$ (b) $(n+1) \times (n+1)$ (c) $n \times n$ (d) $2n \times 2n$
3. For accurate load flow calculations on large power systems, the best method is..... CO2-U
(a) Gauss Seidal (b) Newton Raphson (c) Fast Decoupled (d) Gauss Elimination
4. Which of the following matrix is used for load flow studies? CO2-U
(a) Impedance matrix (b) Jacobian Matrix
(c) Admittance matrix (d) Sparse matrix
5. Which among these is the most severe fault? CO3-R
(a) L-G fault (b) L-L-G fault (c) L-L fault (d) Symmetrical fault
6. Which among the following methods are generally used for the calculation of symmetrical faults? CO3- R
(a) Norton theorem (b) Thevenin's theorem
(c) Kirchhoff's laws (d) All of these


7. What is the value of zero sequence impedance in line to line faults? CO4- U
 (a) $Z_0 = 1$ (b) $Z_0 = \infty$ (c) $Z_0 = 3 Z_n$ (d) $Z_0 = 0$
8. The value of the zero sequence impedance is... CO4- R
 (a) 0 (b) $Z+3n$ (c) $Z+2n$ (d) Z
9. By using which component can the transient stability limit of a power system be improved? CO5- R
 (a) Series resistance (b) Series capacitor (c) Series inductor (d) Shunt resistance
10. The critical clearing time of a fault in power system is related to CO5- R
 (a) Reactive power limit (b) Short circuit limit
 (c) Steady-state stability limit (d) Transient stability limit

PART – B (5 x 2= 10 Marks)

11. Give the benefits of deregulation of power system CO1- R
12. What do you mean by flat voltage start? CO2- R
13. What are the major causes of fault in power system? CO3 -R
14. Write the symmetrical components of three phase system. CO4 -R
15. Draw the power-angle curve. CO5 -U

PART – C (5 x 16= 80Marks)

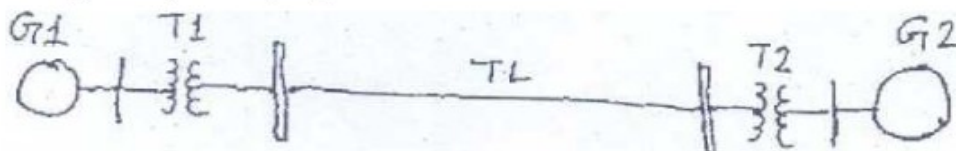16. (a) (i) Draw the structure of an electrical power system and describe the components of the system with typical values. CO1- U (12)
 (ii) write short notes on Deregulation of power system CO1- U (4)
- Or
- (b) choosing a common base of 20 MVA, compute the per unit impedance (reactance) of the components of the power system shown in Fig. and draw the positive sequence impedance (reactance) diagram. CO1- U (16)



Gen 1 : 20 MVA, 10.5 kV, $X'' = 1.4 \text{ Ohm}$
 Gen 2 : 10 MVA, 6.6 kV, $X'' = 1.2 \text{ Ohm}$
 Tr 1 : 10 MVA, 33/11 kV, $X = 15.2 \text{ Ohm}$ per phase on HT side
 Tr 2 : 10 MVA, 33/6.2 kV, $X = 16.0 \text{ Ohm}$ per phase on HT side
 Transmission line : 22.5 Ohms per phase

17. (a) With neat flow chart explain the computational procedure for load flow solution using Gauss Seidal method when the system contains all types of buses CO2- U (16)

Or


- (b) With neat flow chart explain the computational procedure for load flow solution using Fast Decoupled method when the system contains all types of buses CO2- U (16)

18. (a) Asymmetrical fault occurs on bus 4 of system shown in fig. compute the fault current, post fault voltage, line flow. CO3- App (16)

Generator $G_1, G_2 = 100 \text{ MVA}, 20 \text{ KV}, X^+ = 15 \%$


Transformer $T_1, T_2 = X_{\text{leak}} = 9 \%$

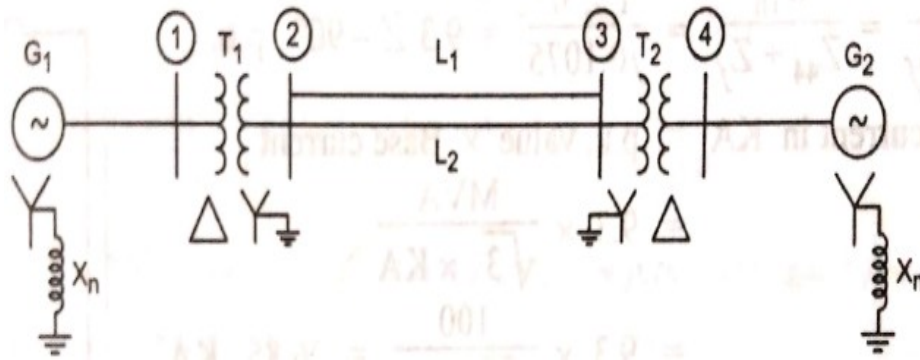Transmission line $L_1, L_2 = X^+ = 10 \%$



Or

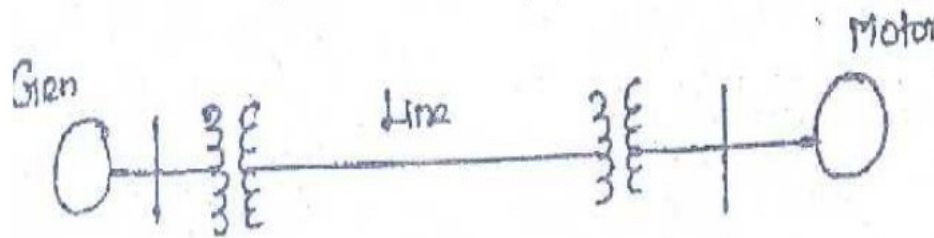- (b) A synchronous generator and a synchronous motor each rated 25 MVA, 11 kV having 15% sub-transient reactance are connected through transformers and a line as shown in fig. The transformers are rated 25 MVA, 11/66 KV and 66/11 kV with leakage reactance of 10% each. The line has a reactance of 10% on a base of 25 MVA, 66 kV. The motor is drawing 15 MW at 0.5 power factor leading and a terminal voltage of 10.6 KV. When a symmetrical 3 phase fault occurs at the motor terminals. Find the sub-transient current in the generator, motor and fault. CO3- App (16)



19. (a) Derive the expression for fault current in Line-to-Line fault on an unloaded generator in terms of symmetrical components CO4- U (16)

Or

- (b) A salient pole generator without dampers is rated 20 MVA, 13.8 kV and has a direct axis sub transient reactance of 0.25 pu. The negative and zero sequence reactances are, respectively, 0.35 and 0.10 pu. The neutral of the generator is solidly grounded. Determine the sub transient current in the generator and the line-to-line voltages for sub transient conditions, when a single line-to-ground fault occurs at the generator terminals with the generator operating unloaded at rated voltage. Neglect resistance CO4- App (16)
20. (a) Derive the swing equation for a single machine connected to infinite bus system. State the assumptions if any and state the usefulness of this equation. Neglect the damping. CO5- U (16)
- Or
- (b) Derive the power angle equation for a SMIB system. Also draw the power-angle curve CO5- U (16)